



Make plots:

- $V_{wyS} = f(V_{weS})$ , ie. a joint plot of four functions for common-mode input voltage  $V_{weS}$  for four configurations: A, B, C and D.
- $I_E = f(V_{weS})$ , ie. a joint plot of  $I_E$  as a function of the common-mode input voltage  $V_{weS}$  for four configurations: A, B, C and D.

3) For each configuration A, B, C, D, based on results of measurements it should be calculated differential gain  $K_r$ , common-mode gain  $K_s$ , and CMRR coefficient. The differential gain  $K_r$  should be calculated as a slope of a linear function  $V_{wyR} = f(V_{weR})$ , whereas the common-mode gain  $K_s$  as a slope of a linear function  $V_{wyS} = f(V_{weS})$ . The CMRR coefficient is to be calculated as a ratio of the differential gain  $K_r$  to the common-mode gain  $K_s$  and should be expressed in dB, ie.  $CMRR = 20 \log \left| \frac{K_r}{K_s} \right|$ .

Configuration:	A: $R_E, R_C$	B: $R_E, R'_C$	C: $R_{E1}, R_C$	D: $R_{E2}, R_C$
$K_r, [V/V]$				
$K_s, [V/V]$				
$CMRR, [dB]$				

4) Using the schematics of the amplifier in configuration A and B, calculate: the operation point of T1 and T2, value of current  $I_E$ , and the differential voltage gain  $K_r$ . Compare the measurement results with the calculated values for  $I_E$  and  $K_r$ .

In calculations assume:  $V_{CC} = 12 \text{ V}$ ,  $V_{BE} = 0.7 \text{ V}$ ,  $R_C = 12 \text{ k}\Omega$ ,  $R'_C = 2 \text{ k}\Omega$ ,  $R_E = 12 \text{ k}\Omega$ ,  $R_e = 385 \Omega$ .

**Operation point for configuration A:**  $I_E = \frac{V_{CC} - V_{BE}}{R_E + \frac{R_e}{2}}$ ,  $V_C = V_{CC} - \frac{R_C I_E}{2}$ ,

**Operation point for configuration B:**  $I_E = \frac{V_{CC} - V_{BE}}{R_E + \frac{R_e}{2}}$ ,  $V_C = V_{CC} - \frac{R'_C I_E}{2}$

in addition calculate:  $g_m = \frac{I_E}{2 \cdot V_T} = \dots\dots\dots$ ,  $g_m^* = \frac{g_m}{2(1 + R_e \cdot g_m)} = \dots\dots\dots$

differential voltage gain for config. A:  $K_r = -2 R_C g_m^*$ , differential voltage gain for config. B:  $K_r = -2 R'_C g_m^*$ .

**Attention: compare measured values for  $V_{we} = 0$ .**

Configuration:	A: $R_E, R_C$		B: $R_E, R'_C$	
	calculated	measured	calculated	measured
$I_E, [\text{mA}]$				
$V_C, [\text{V}]$				
$K_r, [V/V]$				

**For all measurements give your own conclusions and observations. Compare circuits between each other and comment on the compliance calculations with the measurements.**