

# Examination of the input amplifier stage in operational amplifier

# 1A

## 1. Introduction

In this exercise an input stage (e.g. differential amplifier) of the operational amplifier is examined. The measurement system allows to measure basic parameters of the differential amplifier made of bipolar transistors and allows changing the configuration of the differential pair. By means of switches, you can select one of the variants of the current source that biases the transistors, as well as the type of load of the transistors.

**Before starting the exercise, please read the theory about the principles of operation of the differential amplifier (included in this manual).**

## 2. Measurements

Perform measurements of the differential amplifier in the following configurations:

- A. current source — resistor  $R_E$ , load — resistor  $R_C$ ;
- B. current source — resistor  $R_E$ , load —  $R'_C$ ;
- C. current source — transistor with resistor  $R_{E1}$ , load — resistor  $R_C$ ;
- D. current source — transistor with resistor  $R_{E2}$ , load — resistor  $R_C$ ;

**NOTE: Every time the configuration A-D is changed, the circuit must be balanced.** To do this, depress the switch K1 and set the input voltage equal to 0 mV using potentiometer P1. For such a condition, set the same voltages at the collectors of transistors  $T_1$  i  $T_2$  using the potentiometer P3 marked "RESET".

For each configuration, A-D, take measurements of static characteristics when excited by:

- 1) differential input voltage (the switch K1 pressed),
- 2) common-mode input voltage (the switch K1 depressed).

In the first case, measure the voltages at the collectors of transistors  $T_1$  and  $T_2$  ( $V_{WY1}$ ,  $V_{WY2}$ ) as a function of the input differential voltage  $V_{WER}$  (the switch K1 pressed). In addition, for the same values of the input voltage measure the current  $I_E$  (the right gauge). The input voltage must be changed in the range [-150mV, +150mV], using the potentiometer P2. Value of the input voltage can be read from the left gauge, the reading multiply by 10 and the result is in mV.

In the second case (for common-mode input), measure the voltage at the collectors of transistors  $T_1$  and  $T_2$  ( $V_{WY1}$ ,  $V_{WY2}$ ) as a function of the input common-mode voltage  $V_{WES}$  (the switch K1 pressed). In addition, for the same values of the input voltage measure the current  $I_E$ . The input voltage must be changed in the range [-5V, +5V], using the potentiometer P2. Value of the input voltage can be read from the left gauge, the reading multiply by 2 and the result is in V.

Pressing the switch marked:  $R_E$ ,  $R_{E1}$ ,  $R_{E2}$ ,  $R_C$ ,  $R'_C$ ,  $R_D$  will activate the selected configuration. To complete settings of a required configuration, press one of the switches:  $R_E$ ,  $R_{E1}$ ,  $R_{E2}$  (black color) and one of the switches:  $R_C$ ,  $R'_C$ ,  $R_D$  (white color).

## 3. Results elaboration

1) The results of measurements of the differential amplifier in configurations: A, B, C and D to be presented in plots:

-  $V_{WYR} = f(V_{WER})$  ie. a joint plot of  $V_{WYR}$  as a function of the differential input voltage  $V_{WER}$  for the four configurations: A, B, C and D.

-  $I_E = f(V_{WER})$  ie. a joint plot of  $I_E$  as a function of the differential input voltage  $V_{WER}$  for the four configurations: A, B, C and D.

-  $I_E = f(V_{WES})$  ie. a joint plot of  $I_E$  as a function of the common-mode input voltage  $V_{WES}$  for the four configurations: A, B, C and D.

2) Based on the results of measurements calculate: differential voltage gain  $K_r$ , common-mode voltage gain  $K_s$ , and value of CMRR coefficient.

3) Using the schematics of the amplifier in configuration A and B, calculate: the operation point of  $T_1$  and  $T_2$ , value of current  $I_E$ , and the differential voltage gain  $K_r$ . Compare the measurement results with the calculated values for  $I_E$  and  $K_r$ .

Include your own conclusions and observations, compare amplifiers with one another, as well as comment on the compliance of theoretical calculation results with measurements.

## 4. Principle of operation and theory

A simplified schematic of a differential amplifier (without switches for configuration changes and potentiometers for input voltage regulation) is shown in Fig. 1.

The differential amplifier is composed of two symmetrical branches containing transistors  $T_1$  and  $T_2$ .

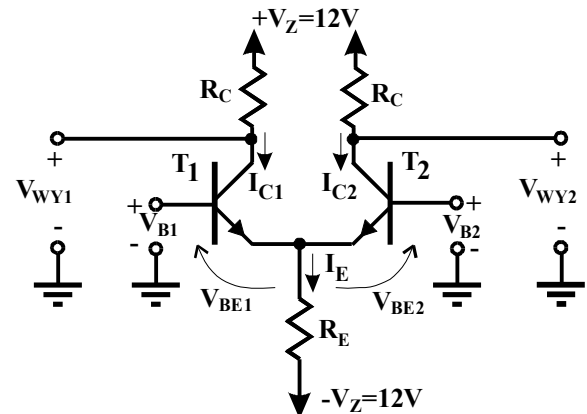


Fig. 1. Simplified schematic of a differential amplifier.

Principle of operation of the amplifier is as follow. If the base voltage  $V_{B1}$  of transistor  $T_1$  is increased to positive value, and the base voltage of transistor  $T_2$  is  $V_{B2}=0$ , then the collector current  $I_{C1}$  of transistor  $T_1$  increases. At the same time the collector current  $I_{C2}$  of transistor  $T_2$  decreases. The situation reverses when the voltage polarity is opposite. In the amplifier the sum of transistors' emitter currents is always equal to the current  $I_E$ , which flows through the resistor  $R_E$ , thus:

$$I_{E1} + I_{E2} = I_E \quad (1)$$

If the resistance  $R_E$  is sufficiently large, the current  $I_E$  is independent of voltages at the bases of transistors  $T_1$  and  $T_2$ . Therefore, it is preferred to use a current source instead of a resistor  $R_E$ . Using the Kirchhoff's current law one can formulate the following equations:

$$\begin{aligned} V_{BE1} &= V_{B1} - V_E \\ V_{BE2} &= V_{B2} - V_E \end{aligned} \quad (2)$$

After removing  $V_E$  from (2), it is achieved:

$$V_{WER} = V_{B1} - V_{B2} = V_{BE1} - V_{BE2} \quad (3)$$

The voltage  $V_{WER}$  is called a differential input voltage. It is seen from (3) that the differential input voltage  $V_{WER}$  is independent of  $R_E$ . Therefore the differential voltage gain  $K_r$  is also independent of  $R_E$ . The schematic of the amplifier with unsymmetrical input voltage is presented in Fig. 2.

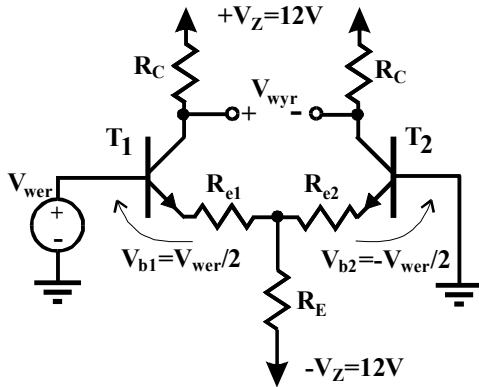


Fig. 2. Differential amplifier with unsymmetrical input and symmetrical output.

In circuit, shown in Fig. 2, the transistor  $T_1$  works in an emitter follower configuration. The signal from  $T_1$  emitter is passed to transistor  $T_2$ , which works in a common base configuration. For sufficiently large resistance  $R_E$ , instantaneous changes in emitter currents of both transistors are equal and opposite. Hence voltages controlling both transistors are almost identical (for a perfect current source instead of  $R_E$ , and identical transistors  $T_1$  and  $T_2$ ). Each of these voltages is half of the input voltage  $V_{wer}$ . Therefore, a differential amplifier has a feature of automatic rebalancing of the input voltage controlling both transistors. As a result, the gain of each branch of the amplifier is equal to half the gain of the entire circuit.

#### 4.1. The region of linear operation of the differential amplifier

Fig. 3 shows typical static characteristics of a differential amplifier. It can be seen that there is a range of relatively linear operation. The transfer characteristics of the transistors are linear in the vicinity of a quiescent point of the amplifier, i.e. midpoint corresponding to a situation where  $V_{B1} = V_{B2}$ . The region of linear operation of the amplifier corresponds to the difference of the input voltages of approximately 50 mV. This range is thus very small. If the linear range needs to be expanded, this can be achieved, including additional resistors  $R_{e1}$  and  $R_{e2}$  between the emitters of the transistors and the connection point of the resistor  $R_E$  (as shown in Fig. 2). The additional resistors introduce a negative feedback that extends a range of linearity of equivalent transconductance  $g_m^*$  of the amplifier. The influence of the resistances  $R_e = R_{e1} = R_{e2}$  on the linear range is shown in Fig. 4.

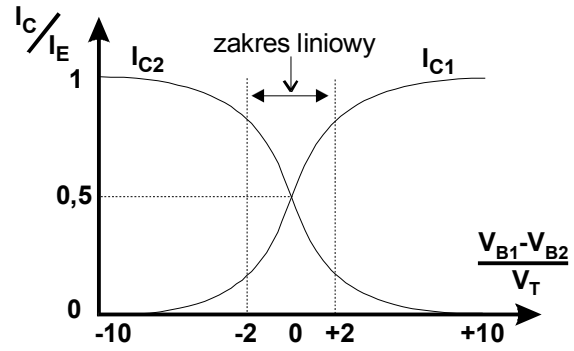


Fig. 3 Static characteristics of a differential amplifier.

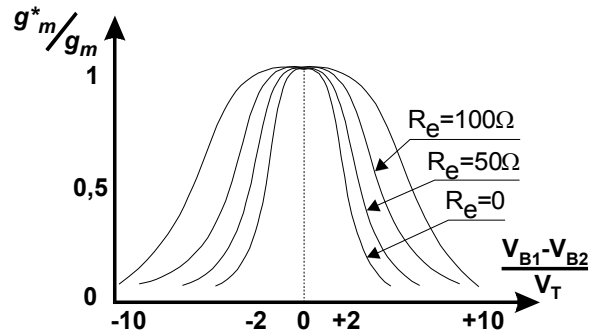


Fig. 4 The influence of the resistances  $R_e = R_{e1} = R_{e2}$  on the linear range of the amplifier transconductance  $g_m^*$ .

Under assumption that  $R_{e1} = R_{e2}$ , the equivalent transconductance  $g_m^*$  of the amplifier, working with unsymmetrical output, can be calculated from:

$$g_m^* = \frac{g_m}{2(1 + R_e g_m)} \quad (4)$$

where  $g_m = I_C / V_T$ ,  $V_T = 25,8 mV$ .

#### 4.2. The role of resistor $R_E$ in a differential amplifier

For equal in amplitude and in-phase input voltages  $V_{B1}$  and  $V_{B2}$  (common-mode), or for similar changes of transistors parameters (eg. caused by changes of ambient temperature) there is a strong negative feedback on a common resistance  $R_E$ . This feedback is the stronger the higher is the resistance  $R_E$ . On the other hand, when the amplifier is excited by a differential voltage, changes in currents of both transistors are opposite and reduce at the resistance  $R_E$ . Therefore in this case the resistance does not affect the output voltage of the amplifier. Consequently, the gain for a differential voltage is much greater than for a common-mode one. The differential gain depends only on resistance  $R_C$  and  $R_e$ , whereas the common-mode gain depends on resistance  $R_C$ ,  $R_e$  and  $R_E$ , namely:

$$K_r = \frac{\Delta V_{WYR}}{\Delta V_{WER}} = -2R_C g_m^* \quad (5)$$

$$K_s = \frac{\Delta V_{WY1}}{\Delta V_{WES}} = -\frac{R_C g_m}{1 + (2R_E + R_e)g_m} \quad (6)$$

The equation (5) was derived based on equation (4), which defines the transconductance for a whole differential amplifier (the gain is equal to the product of the transconductance  $g_m^*$  and the load resistance  $R_C$ ).

#### 4.3. Common-mode operation of a differential amplifier

The common-mode operation of a differential amplifier is when both input voltages are equal  $V_{B1} = V_{B2}$ . In this case the

voltages controlling the transistors will be reduced by the amount of a drop voltage across the resistor  $R_E$ . Therefore, the gain for a common mode voltages is strongly dependent on resistance  $R_E$ . From equation (6) it can be seen that the greater the resistance  $R_E$  is, the smaller the gain  $K_S$  is. In practice, all the disturbance signals are common mode, eg. thermal drift that alters the operating points of transistors  $T_1$  and  $T_2$ . On the other hand differential signal carries useful information. It can be concluded that an ideal differential amplifier should have zero common mode gain.

#### 4.4. Calculation of operation points of the transistors

The operation points of the transistors can be calculated based on the schematic in Fig. 2. In the quiescent state of the amplifier (the absence of the input voltage  $V_{wer} = 0$ ) the following equations are valid:

$$\begin{aligned} V_{BE1} + I_E R_E + I_{C1} R_{e1} &= V_z \\ I_{C1} &= I_E / 2 \end{aligned} \quad (7)$$

hence:

$$\begin{aligned} I_E &= \frac{V_z - V_{BE}}{R_E + R_{e1}/2}; \quad I_{C1} = I_{C2} = I_E / 2 \\ V_{C1} &= V_{C2} = V_z - R_C I_E / 2 \end{aligned} \quad (8)$$

The calculation of  $I_E$  for a configuration with a current source using the transistor  $T_3$ , can be performed as follow (refer to Fig. 5):

$$V_{B3} = -\frac{R_7}{R_7 + R_8} V_z; \quad I_E \cong I_{E3} = \frac{V_z + V_{B3} - V_{BE}}{R_{E1}} \quad (9)$$

assume  $V_{BE} = 0,65$  V.

#### 4.5. Common-mode rejection ratio — CMRR

In pursuit to perfection, the differential amplifiers are designed in such a way to get the smallest common-mode gain. The parameter that characterizes the relationship between the useful differential gain to the disadvantageous common-mode gain is called CMRR (*Common Mode Rejection Ratio*):

$$CMRR = \frac{K_r}{K_{rs}} = \frac{\Delta V_{WYR} / \Delta V_{WER}}{\Delta V_{WYR} / \Delta V_{WES}} = \frac{\Delta V_{WES}}{\Delta V_{WER}} \quad (7)$$

In practice, it is more convenient to determine CMRR using the rightmost component of equation (7). This definition says, that CMRR is a ratio of the common-mode input voltage to the differential input voltage, which generates the same differential output voltage at the output. If the differential amplifier is perfectly symmetric, CMRR is equal to infinity. In a real circuit, however, CMRR value is limited and increases with increasing of the resistance  $R_E$ . Therefore, in order to obtain the best CMRR, it is required that the resistance  $R_E$  has the largest possible value. It is also necessary that the two transistors have identical parameters, in particular the current gain factor  $\beta$ .

#### 4.6. Current source biasing emitters of an amplifier

As stated, it is possible to achieve good characteristics of the differential amplifier provided that resistance  $R_E$  is high. Increasing the value of this resistor is in practice limited by the supply voltage. It is possible, however, the application of a current source in place of the resistor. The simplest current source can be realized as a single transistor in the configuration shown in Fig. 5.

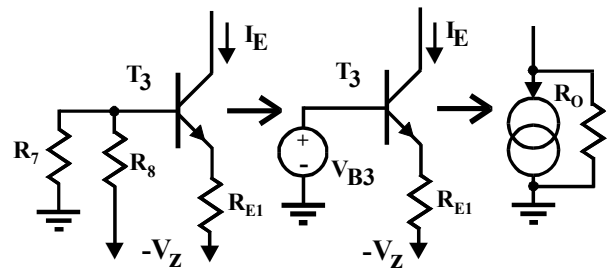


Fig. 5. An example of a current source implemented using a single transistor.

A typical value of the output resistance  $R_O$  of the source shown in Fig. 5 is equal to a few dozen  $M\Omega$ .

#### 5. Parameters of the components used in the circuit

$R_1=110\Omega$	$R_5=820\Omega$	$R_C=12k\Omega$
$R_2=110\Omega$	$R_6=820\Omega$	$R'_C=2k\Omega$
$R_3=8,2k\Omega$	$R_7=2k\Omega$	$R_E=12k\Omega$
$R_4=8,2k\Omega$	$R_8=910\Omega$	$R_{E1}=3,13k\Omega$
$R_{E2}=6,36k\Omega$	$R_P=490\Omega$	$R_W=4,9k\Omega$
$R_{5DO}=5,18k\Omega$	$P_1=2,2k\Omega$	$R_{e1}=R_{e2}=$
$P_2=10k\Omega$	$P_3$ "ZER"=470 $\Omega$	$P_3$ "ZER"/2

#### Literature:

- [1] Z. J. Staszak, J. Glinianowicz, D. Czarnecki "Materiały pomocnicze do przedmiotu Układy Elektroniczne Liniowe".
- [2] A. Guziński, "Liniowe elektroniczne układy analogowe" WNT 1992.
- [3] S. Soclof, "Zastosowania analogowych układów scalonych", WKŁ 1991.