

LABORATORY OF ELECTRONICS

1B	Script exercise No.:	Consecutive exercise No.:	Lab team members: 1. 2. 3.
Subject: Operational amplifier (dynamic characteristics)		DEAN GROUP:	LAB GROUP:
Planned lab exercise execution date:		Real lab exercise execution date:	Lab exercise report submission date:
			Grade:

2.1. Measurements of a differential pair (circuit A)

2.1.1. Differential input mode measurements, $f = 1\text{kHz}$; measurements of the harmonic distortion h :

DIFF/CM released, KRE released (V_{we} – input voltage; V_{wy} – output voltage)

V_{we} [mV]	5	10	15	20	25	30	35	40	45	50
h [%]										

Note: The input voltage meter measures the RMS (Root Mean Square) voltage value but the oscilloscope - the maximum value. In order to compare them for example multiply by $\sqrt{2}$ the value of the input voltage meter reading.

Measurement of the differential mode gain K_{uDIFF} and input resistance R_{in} , $f = 1\text{kHz}$:

V_{we} [mV]	V_{wy} [V]	$K_{uDIFF} = V_{wy}/V_{we}$ [V/V]	measured R_{in} : V_{wy} [V]
10			

2.1.2. Common input mode measurements, $f = 1\text{kHz}$; measurement of the common mode gain K_{uCM} and input resistance R_{in} :

DIFF/CM pressed, KRE released

V_{we} [V]	V_{wy} [V]	$K_{uCM} = V_{wy}/V_{we}$ [V/V]	measured R_{in} : V_{wy} [V]
1			

2.2. Measurements of the magnitude frequency response of the amplifier (circuit B) for resistor feedbacks 10k/10k and 1k/10k, $K_u = V_{wy}/V_{we}$

10k/10k				1k/10k			
V_{we} [mV]	25		20·log K_u	V_{we} [mV]	20		20·log K_u
f [kHz]	V_{wy} [mV]	K_u [V/V]		f [kHz]	V_{wy} [mV]	K_u [V/V]	
0.11				0.11			
1.0				1.0			
20.0				2.0			
50.0				3.0			
100.0				5.0			
125.0				6.0			
150.0				8.0			
200.0				10.0			
250.0				12.0			
300.0				14.0			
400.0				16.0			
500.0				18.0			
-				20.0			
-				30.0			
-				40.0			
-				50.0			
-				75.0			
-				100.0			
-				200.0			
-				400.0			
f_{H3dB} [kHz]				f_{H3dB} [kHz]			
f_T [kHz] dla $V_{wy} = 25\text{ mV}$				f_T [kHz] dla $V_{wy} = 20\text{ mV}$			

Measurements of the 3dB cutoff frequencies and the unity-gain frequencies:

$$f_{L3dB} - \text{lower 3dB cutoff frequency, i.e.: } K_u(f_{L3dB}) = 0.707 \cdot K_u(f=1kHz),$$

$$f_T - \text{unity-gain frequency, i.e.: } V_{wy}(f_T) = V_{we} \text{ or } K_u(f_T) = 1.$$

3. Elaboration of the results

1) Plot a graph of nonlinear distortion h as the function of the input voltage V_{we} for the circuit A (differential input mode).

2) For a differential pair calculate analytically the operating point of transistors, the small-signal gain and the input resistance.

For the calculations assume: $V_{CC} = 12V$, $V_{EE} = -12V$, $V_{BE} = 0.7V$, $V_T = 25mV$, $\beta = 120$, $R_{EE} = 10 k\Omega$, $R_E = 100 \Omega$, $R_C = 5.1 k\Omega$, $R_{SZERDIFF} = 5.1 k\Omega$, $R_{SZERCM} = 1500 k\Omega$, $R_{GEN} = 50 \Omega$, $R_{BUF} = 1000 k\Omega$

$$\text{Operating point: } I_{EE} = \frac{-V_{EE} - V_{BE}}{R_{EE} + \frac{R_E}{2}} = \dots\dots\dots, \quad \alpha = \frac{\beta}{\beta + 1} = \dots\dots\dots, \quad I_C = \alpha \cdot 0.5 \cdot I_{EE} = \dots\dots\dots, \quad V_C = V_{CC} - R_C I_C = \dots\dots\dots$$

Auxiliary calculations:

$$g_m = \frac{I_C}{V_T} = \dots\dots\dots, \quad r_\pi = \frac{\beta}{g_m} = \dots\dots\dots, \quad r_e = \frac{r_\pi}{\beta + 1} = \dots\dots\dots$$

For the calculations use the following formulas:

Differential input mode	Common input mode
Input resistance (theory) R_{IN}	
$R_{INDIFF} = 2(\beta + 1)(R_E + r_e)$	$R_{INCM} = \frac{1}{2}(\beta + 1)(2R_{EE} + R_E + r_e)$
Input resistance (measured) R_{IN}	
$R_{INDIFF} = 2 \frac{V_{wy'}}{V_{wy} - V_{wy'}} \cdot R_{SZER} - R_{GEN}$	$R_{INCM} = \frac{V_{wy'}}{V_{wy} - V_{wy'}} \cdot R_{SZER} - R_{GEN}$
Small-signal gain K_u	
$K_{uDIFF} = \frac{R_{INDIFF}}{R_{INDIFF} + 2R_{GEN}} \cdot \frac{\alpha \cdot R_C \cdot R_{BUF}}{R_C + R_{BUF}} \cdot \frac{1}{r_e + R_E}$	$K_{uCM} = \frac{R_{INCM}}{R_{INCM} + 2R_{GEN}} \cdot \frac{\alpha \cdot R_C \cdot R_{BUF}}{R_C + R_{BUF}} \cdot \frac{1}{2R_{EE} + r_e + R_E}$

Compare the calculation results with the results of measurements in the table below:

	Differential input mode		Common input mode	
	theory	measured	theory	measured
$R_{IN} [k\Omega]$				
K_u				

Moreover, calculate the Common Mode Rejection Ratio coefficient: $CMRR = 20 \log \frac{K_{uDIFF}}{K_{uCM}} = \dots\dots\dots$

3) Plot the measured characteristics of the amplifier $20 \cdot \log |K_u|$ for feedback resistors 10k/10k, 1k/10k on separate graphs (linear vertical axis, logarithmic horizontal axis). Mark the 3dB cutoff frequency and the unity-gain frequency.

Write your own conclusions and observations for all measurements in the exercise. Compare circuits and write comments on differences between calculations and measurements.