

# LABORATORY OF ELECTRONIC CIRCUITS

|                                 |                              |                      |
|---------------------------------|------------------------------|----------------------|
| Laboratory exercise no.:        | Consecutive protocol number: | Name and surname:    |
| <b>2</b>                        |                              | 1.<br>2.<br>3.       |
| <b>Title: Negative feedback</b> |                              |                      |
| Day of week:                    | Date of the measurements:    | Date of elaboration: |
|                                 | <b>Grade:</b>                |                      |

**2.1. Measurement of the following parameters of the amplifier for different feedback configurations: low and high 3-dB frequencies ( $f_{L3dB}$ ,  $f_{H3dB}$ ), center frequency ( $f_0$ ), input and output resistances ( $R_{in}$ ,  $R_{out}$ ), nonlinear distortions ( $h$ ). Initial conditions of the measurements:  $f_{in} = 18 \text{ kHz}$ ,  $V_o = 300 \text{ mV}_{RMS}$**

| Amplifier's configuration  | A (open loop) | B (closed loop 1) | C (closed loop 2) |
|--|---------------|-------------------|-------------------|
| input voltage $V_s$ [mV]   |               |                   |                   |
| $f_{L3dB}$ (at $V_o = 300/\sqrt{2} \approx 212 \text{ mV}_{RMS}$ ) [kHz] |               |                   |                   |
| $f_{H3dB}$ (at $V_o = 300/\sqrt{2} \approx 212 \text{ mV}_{RMS}$ ) [kHz] |               |                   |                   |
| center frequency $f_0 = \sqrt{f_{L3dB} \cdot f_{H3dB}}$ [kHz]            |               |                   |                   |
| gain at center frequency $K_u(f_0)$ [V/V]                                |               |                   |                   |
| output voltage $V_o'$ for $R_{in}$ measurement [mV]                      |               |                   |                   |
| output voltage $V_o'$ for $R_{out}$ measurement [mV]                     |               |                   |                   |
| nonlinear distortion $h$ [%]   |               |                   |                   |

**2.2. Measurement of an amplitude characteristic of the amplifier for different feedback configurations (measurements are conducted by point-by-point method).**

Initial conditions of the measurements: for each amplifier's configuration, set initially  $f_{in} = 18 \text{ kHz}$ , and set  $V_s$  at which  $V_o$  is  $300 \text{ mV}_{RMS}$ .

| A (open loop) |       |       |                       | B (closed loop 1) |       |       |                       | C (closed loop 2) |       |       |                       |
|---------------|-------|-------|-----------------------|-------------------|-------|-------|-----------------------|-------------------|-------|-------|-----------------------|
| $f$           | $V_o$ | $K_u$ | $20 \cdot \log  K_u $ | $f$               | $V_o$ | $K_u$ | $20 \cdot \log  K_u $ | $f$               | $V_o$ | $K_u$ | $20 \cdot \log  K_u $ |
| [kHz]         | [mV]  | [V/V] |                       | [kHz]             | [mV]  | [V/V] |                       | [kHz]             | [mV]  | [V/V] |                       |
| 1.0           |       |       |                       | 200 Hz            |       |       |                       | 200 Hz            |       |       |                       |
| 2.0           |       |       |                       | 400 Hz            |       |       |                       | 400 Hz            |       |       |                       |
| 4.0           |       |       |                       | 700 Hz            |       |       |                       | 700 Hz            |       |       |                       |
| 7.0           |       |       |                       | 1.0               |       |       |                       | 2.0               |       |       |                       |
| 10.0          |       |       |                       | 2.0               |       |       |                       | 4.0               |       |       |                       |
| 18.0          |       |       |                       | 18.0              |       |       |                       | 18.0              |       |       |                       |
| 50.0          |       |       |                       | 50.0              |       |       |                       | 50.0              |       |       |                       |
| 70.0          |       |       |                       | 100.0             |       |       |                       | 100.0             |       |       |                       |
| 100.0         |       |       |                       | 500.0             |       |       |                       | 500.0             |       |       |                       |
| 120.0         |       |       |                       | 1 MHz             |       |       |                       | 700.0             |       |       |                       |
| 140.0         |       |       |                       | 1.4 MHz           |       |       |                       | 1 MHz             |       |       |                       |
| 170.0         |       |       |                       | 1.7MHz            |       |       |                       | 1.2 MHz           |       |       |                       |
| 200.0         |       |       |                       | 2 MHz             |       |       |                       | 1.5 MHz           |       |       |                       |
| 500.0         |       |       |                       | 3 MHz             |       |       |                       | 2 MHz             |       |       |                       |

### 3. Data elaboration

1) Plot the measured characteristics  $20 \log |K_u|$  on separate graphs (vertical axis is linear, horizontal axis is logarithmic).

2) Calculate operating points of the transistors, the amplifier gain and input and output resistances of the amplifier.

Use the following data:  $V_{CC} = 12V$ ,  $V_T = 25mV$ ,  $V_{BE} = 0.7V$ ,  $\beta = 200$ ,  $\alpha = \frac{\beta}{\beta+1}$ ,  $R_{B1} = 51k\Omega$ ,  $R_{B2} = 6.2k\Omega$ ,  $R_{C1} = 8.2k\Omega$ ,

$R_{C2} = 2.2k\Omega$ ,  $R_{E1} = 560\Omega$ ,  $R_{E2} = 1.2k\Omega$ ,  $R_L = 5.1k\Omega$ ,  $R_{Fb} = 18k\Omega$ ,  $R_{Fc} = 36k\Omega$ ,  $R_S = R_L = 1k\Omega$ ,  $R_S = 2k\Omega$

Operating point of the transistor Q1:  $V_{B_1} = V_{CC} \frac{R_{B_2}}{R_{B_1} + R_{B_2}} = \dots\dots\dots$ ,  $I_{C_1} = \frac{V_{B_1} - V_{BE}}{R_{E_1}} = \dots\dots\dots$ ,

$V_{CE_1} = V_{CC} - (R_{C_1} + R_{E_1}) \cdot I_{C_1} = \dots\dots\dots$ ,

Operating point of the transistor Q2:  $V_{B_2} = V_{CC} - R_{C_1} \cdot I_{C_1} = \dots\dots\dots$ ,  $I_{C_2} = \frac{V_{B_2} - V_{BE}}{R_{E_2}} = \dots\dots\dots$ ,

$V_{CE_2} = V_{CC} - (R_{C_2} + R_{E_2}) \cdot I_{C_2} = \dots\dots\dots$

Auxiliary equations:

$g_{m_1} = \frac{I_{C_1}}{V_T} = \dots\dots\dots$ ,  $r_{\pi_1} = \frac{\beta}{g_{m_1}} = \dots\dots\dots$ ,  $r_{e_1} = \frac{r_{\pi_1}}{\beta + 1} = \dots\dots\dots$ ,  $R_{1_B} = \frac{R_{E_1} \cdot R_{F_B}}{R_{E_1} + R_{F_B}} = \dots\dots\dots$ ,  $R_{2_B} = R_{E_1} + R_{F_B} = \dots\dots\dots$ ,

$g_{m_2} = \frac{I_{C_2}}{V_T} = \dots\dots\dots$ ,  $r_{\pi_2} = \frac{\beta}{g_{m_2}} = \dots\dots\dots$ ,  $r_{e_2} = \frac{r_{\pi_2}}{\beta + 1} = \dots\dots\dots$ ,  $R_{1_C} = \frac{R_{E_1} \cdot R_{F_C}}{R_{E_1} + R_{F_C}} = \dots\dots\dots$ ,  $R_{2_C} = R_{E_1} + R_{F_C} = \dots\dots\dots$

For calculations, please use the formulas in the table below. Attention: for configuration B use  $R_{1_B}$  i  $R_{2_B}$  for calculations; for configuration C use  $R_{1_C}$  i  $R_{2_C}$ . You must fill empty fields in the table below.

| A (open loop)  | B (closed loop 1)   | C (closed loop 2) |
|--|---|-------------------|
| Small-signal gain $K_u$  |   |                   |
| $K_u = g_{m_2} \cdot \frac{R_{C_2} R_L}{R_{C_2} + R_L} \cdot \frac{\alpha \cdot R_{C_1} \cdot r_{\pi_2}}{R_{C_1} + r_{\pi_2}} \cdot \frac{1}{r_{e_1} + R_{E_1}} \cdot \frac{R_{in}}{R_{in} + R_S}$ | $A' = g_{m_2} \cdot \left( \frac{1}{R_{C_2}} + \frac{1}{R_L} + \frac{1}{R_2} \right)^{-1} \cdot \frac{\alpha \cdot (R_{C_1} \cdot r_{\pi_2})}{R_{C_1} + r_{\pi_2}} \cdot \frac{1}{r_{e_1} + R_1} \cdot \frac{(r_{e_1} + R_1) \cdot (\beta + 1)}{(r_{e_1} + R_1) \cdot (\beta + 1) + R_S}$ |                   |
|  | $B = \frac{R_{E_1}}{R_{E_1} + R_F}, K_u = A_f = \frac{A'}{1 + A' B}$  |                   |
| Calculation of the input resistance $R_{in}$   |   |                   |
| $R_{in} = \left( \frac{1}{R_{B_1}} + \frac{1}{R_{B_2}} + \frac{1}{(r_{e_1} + R_{E_1}) \cdot (\beta_1 + 1)} \right)^{-1}$   | $R_i = R_S + (\beta + 1) \cdot (r_{e_1} + R_2), R_{if} = R_i \cdot (1 + A' \cdot B), R_{in} = \left( \frac{1}{R_{if} - R_S} + \frac{1}{R_{B_1}} + \frac{1}{R_{B_2}} \right)^{-1}$   |                   |
|  | $R_i = \dots\dots\dots, R_{if} = \dots\dots\dots$   |                   |
| Calculation of the output resistance $R_{out}$   |   |                   |
| $R_{out} = R_{C_2}$  | $R_0 = \left( \frac{1}{R_{C_2}} + \frac{1}{R_L} + \frac{1}{R_2} \right)^{-1}, R_{of} = \frac{R_0}{1 + A' B}, R_{out} = \frac{R_{of} \cdot R_L}{R_L - R_{of}}$   |                   |
|  | $R_0 = \dots\dots\dots, R_{of} = \dots\dots\dots$   |                   |

| Amplifier's configuration  | A (open loop) |          | B (closed loop 1) |          | C (closed loop 2) |          |
|--|---------------|----------|-------------------|----------|-------------------|----------|
|  | theoretical   | measured | theoretical       | measured | theoretical       | measured |
| $K_u$  |               |          |                   |          |                   |          |
| $R_{in} = \frac{V_o'}{V_o - V_o'} \cdot R_S' - R_S$ [kΩ]                 |               |          |                   |          |                   |          |
| $R_{out} = \frac{R_L \cdot R_L'}{R_L \cdot V_o' - V_o' \cdot R_L'}$ [kΩ] |               |          |                   |          |                   |          |
| $f_{L3dB}$ [kHz]   | -             |          | -                 |          | -                 |          |
| $f_{H3dB}$ [kHz]   | -             |          | -                 |          | -                 |          |

**For each measurement result, include your conclusions. Compare the above theoretical results with the measurement results of the real circuits.**