LABORATORY OF ELECTRONIC CIRCUITS										
Laboratory exercise no.: 5	Consecutive number:	e protocol	Name and surname: 1. 2. 3.							
Title: Audio Amplifier										
Day of week:		Date of the measurements:		Date of elaboration:						
		Grade:		1						

## **2.1.** Measurement of the output power, efficiency and total harmonic distortion ratio at several loads $R_0$ and input voltages, f=1kHz:

$V_{we}$	$R_0=4\Omega$				$R_0=6\Omega$				$R_0=10\Omega$						
	Izas	$P_{wy}$	h	Pzas	$P_{str}$	Izas	$P_{wy}$	h	Pzas	$P_{str}$	Izas	$P_{wy}$	h	$P_{\rm zas}$	P <sub>str</sub>
[mV] <sub>RMS</sub>	[mA]	[W]	[%]	[W]	[W]	[mA]	[W]	[%]	[W]	[W]	[mA]	[W]	[%]	[W]	[W]
5															
10															
15															
20															
25															
30															
35															
40															
45															
50															
55															
60															

1) Calculate the power supply:  $P_{zas} = I_{zas} \cdot U_{zas}$ , where  $U_{zas}=15V$  and the power loss:  $P_{str}=P_{zas}-P_{wy}$ . For <u>each</u>  $R_0=4$ , 6, 10 $\Omega$  separately, plot on a single graph:  $P_{zas}(V_{we})$ ,  $P_{wy}(V_{we})$ ,  $P_{str}(V_{we})$  (three graphs). Determine the value of  $V_{we}$ , for which the maximum power loss is observed.

2) Plot on a single graph for all  $R_0=4, 6, 10\Omega$ , the dependency:  $h(V_{we})$ .

## **2.1.** Measurement of the frequency characteristics of the amplifier, $V_{we}$ =10mV<sub>RMS</sub>:

$R_0=4\Omega$		$R_0=$	:6Ω	$R_0=10\Omega$			
f[kHz]	$P_{wy}$ [W]	f[kHz]	$P_{wy}$ [W]	f[kHz]	$P_{wy}$ [W]		

- 1) Plot the frequency characteristics of the amplifier for all  $R_0$ =4, 6, 10 $\Omega$  on a single graph. Use log coordinates for X axis and linear coordinates for Y axis.
- 2)On the basis of the measurements, determine the optimum load resistance  $R_{\rho}$  due to:
  - a) the output power and the efficiency;
  - b) the distortions.

For each measurement results, include your conclusions and observations. Compare the circuits with each other write your own comments to the results.