

# Introduction to Basic Electronic Circuits non-linear circuits

Ph.D., D.Sc. Bogdan Pankiewicz - lecture, WETI PG room EA307

[www.ue.eti.pg.gda.pl/~bpa/ec/](http://www.ue.eti.pg.gda.pl/~bpa/ec/)

# Lecture content

- Distortion and gain measures for non-inertial systems for harmonic excitation
- Differential bipolar pair
- Simple analogue multiplier using differential pair
- Gilbert multiplier
- Selected non-linear circuits

# Literature:

- 1) U. Tietze, C. Schenk, E Gamm „Electronic circuits, handbook for design and applications”, Springer 2002.
- 2) R. L. Geiger, P. E. Allen, N. R. Strader, „VLSI design techniques for analog and digital circuits“, McGraw-Hill 1990.
- 3) P. E. Allen, D. R. Holberg, „CMOS analog circuit design“, Sanders College Publishing, 1987.
- 4) P. R. Gray, R. G. Meyer, ”Analysis and design of analog integrated circuits”, John Wiley & Son, Inc. 1993.
- 5) P. Wambacq, W. Sansen, „Distortion analysis of analog integrated circuits”, Kluwer Academic Publishers, 1998.

# Distortion and gain measures for non-inertial systems for harmonic excitation

For simplicity non-inertial non-linear circuit is assumed. Its transfer function is given by the polynomial:

$$v_{OUT} = f(v_{IN}) = K_0 + K_1 v_{IN} + K_2 v_{IN}^2 + K_3 v_{IN}^3$$

Gain and distortion for single harmonic excitation can be found by substitution:

$$v_{IN} = B \cos(\omega_B t)$$

Components of individual powers:

$$\cos^2 \alpha = \frac{1}{2} + \frac{1}{2} \cos(2\alpha)$$

$$K_1 v_{IN} = K_1 B \cos(\omega_B t)$$

$$\cos^3 \alpha = \frac{1}{4} \cos(3\alpha) + \frac{3}{4} \cos \alpha$$

$$K_2 v_{IN}^2 = K_2 B^2 \cos^2(\omega_B t) = \frac{1}{2} K_2 B^2 + \frac{1}{2} K_2 B^2 \cos(2\omega_B t)$$

$$K_3 v_{IN}^3 = K_3 B^3 \cos^3(\omega_B t) = \frac{1}{4} K_3 B^3 \cos(3\omega_B t) + \frac{3}{4} K_3 B^3 \cos(\omega_B t)$$

# Distortion and gain measures for non-inertial systems for harmonic excitation

$$\begin{aligned}
 v_{OUT} &= f(B \cos(\omega_B t)) = K_0 + K_1 B \cos(\omega_B t) + \frac{1}{2} K_2 B^2 + \frac{1}{2} K_2 B^2 \cos(2\omega_B t) \\
 &+ \frac{1}{4} K_3 B^3 \cos(3\omega_B t) + \frac{3}{4} K_3 B^3 \cos(\omega_B t) \\
 &= K_0 + \frac{1}{2} K_2 B^2 + \left[ K_1 B + \frac{3}{4} K_3 B^3 \right] \cos(\omega_B t) + \frac{1}{2} K_2 B^2 \cos(2\omega_B t) + \frac{1}{4} K_3 B^3 \cos(3\omega_B t)
 \end{aligned}$$

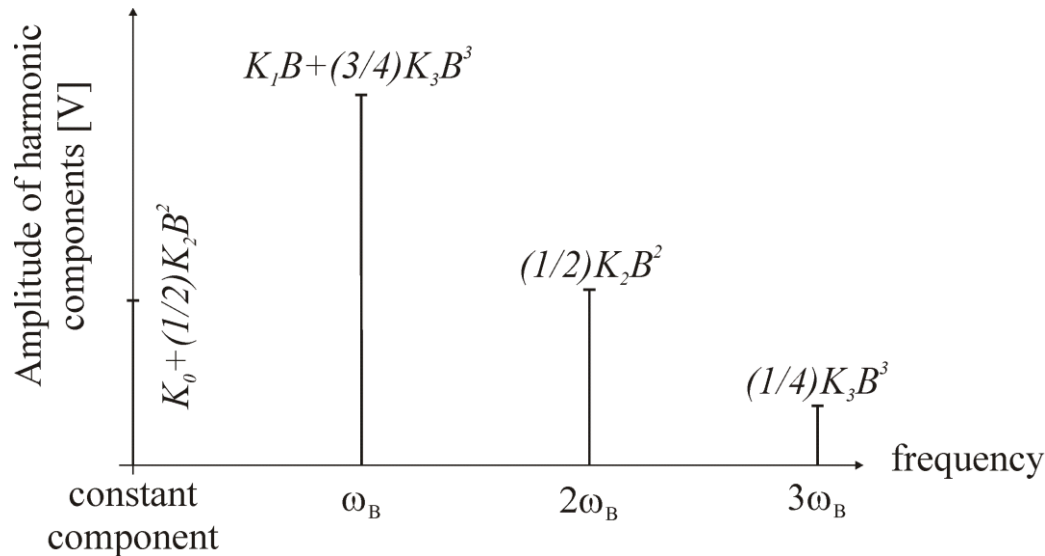


Fig. 1. Harmonic content with for harmonic excitation of non-inertial system described by 3rd degree polynomial.

# Distortion and gain measures for non-inertial systems for harmonic excitation

- Individual powers of a polynomial result in harmonics with frequencies that are multiples of the power of a polynomial.
- The even powers of the polynomial also change the constant component of the output signal and make it dependent on the amplitude of the input signal.
- The amplitudes of individual subsequent harmonics are decreasing with the harmonic number.
- With slight distortion of the processing system, you can approximate its properties by limiting the describing function to the first few powers of the polynomial.

# Bipolar differential pair

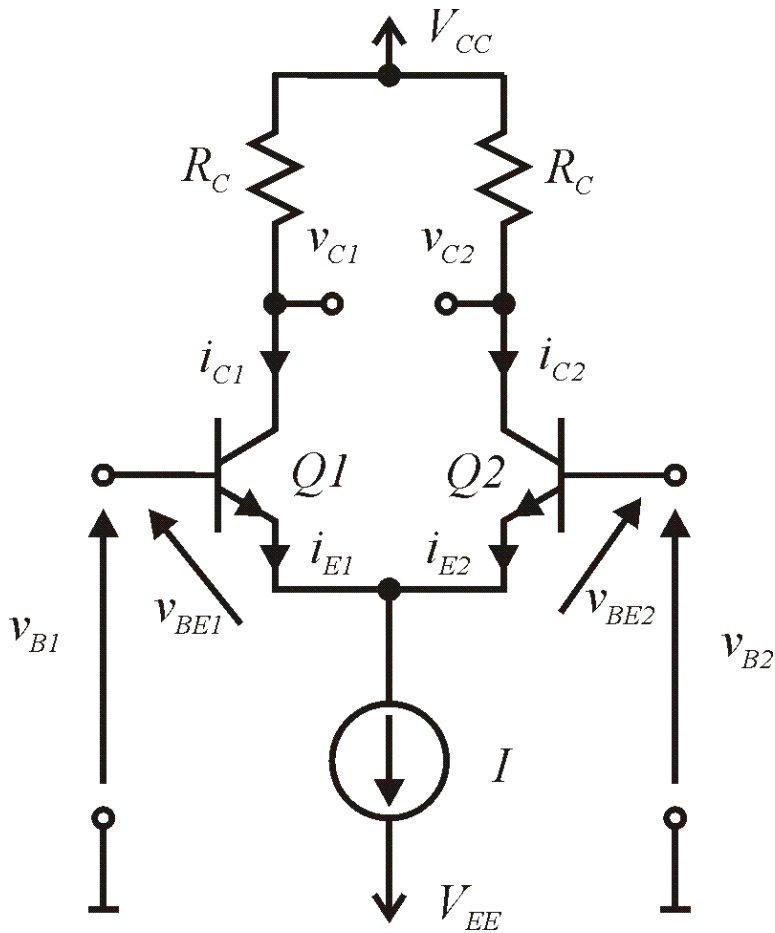


Fig. 2. Bipolar differential pair.

Emitter currents of transistors:

$$i_{E1} = \frac{I_S}{\alpha} e^{\frac{v_{B1} - v_E}{V_T}} \quad i_{E2} = \frac{I_S}{\alpha} e^{\frac{v_{B2} - v_E}{V_T}}$$

hence:

$$\frac{i_{E1}}{i_{E2}} = \frac{\frac{I_S}{\alpha} e^{\frac{v_{B1} - v_E}{V_T}}}{\frac{I_S}{\alpha} e^{\frac{v_{B2} - v_E}{V_T}}} = e^{\frac{v_{B1} - v_{B2}}{V_T}} = e^{\frac{v_{ID}}{V_T}}$$

Together with Kirchhoff's current law, it gives the following equations:

$$\begin{cases} i_{E1} + i_{E2} = I \\ i_{E1} / i_{E2} = e^{v_{ID}/V_T} \end{cases}$$

# The harmonic signal gain

**Def: Gain of the harmonic wave can be defined as the ratio of the amplitude of the first harmonic output signal to the amplitude of the input signal:**

$$A_H(B) = \frac{\text{1-st harmonic amplitude}}{\text{amplitude of input sine wave}} = \frac{\left[ K_1 B + \frac{3}{4} K_3 B^3 \right]}{B} = K_1 + \frac{3}{4} K_3 B^2$$


The above gain is not constant and depends on the amplitude of the input signal. Depending on the sign of the  $K_3$  coefficient, both increase (expansion) and reduction (compression) of the gain can occur.



# Bipolar differential pair, cont.

The solution gives the following results:

$$\begin{cases} i_{E1} = I \left( \frac{1}{1 + e^{-v_{ID}/V_T}} \right) \\ i_{E2} = I \left( \frac{1}{1 + e^{v_{ID}/V_T}} \right) \end{cases}$$

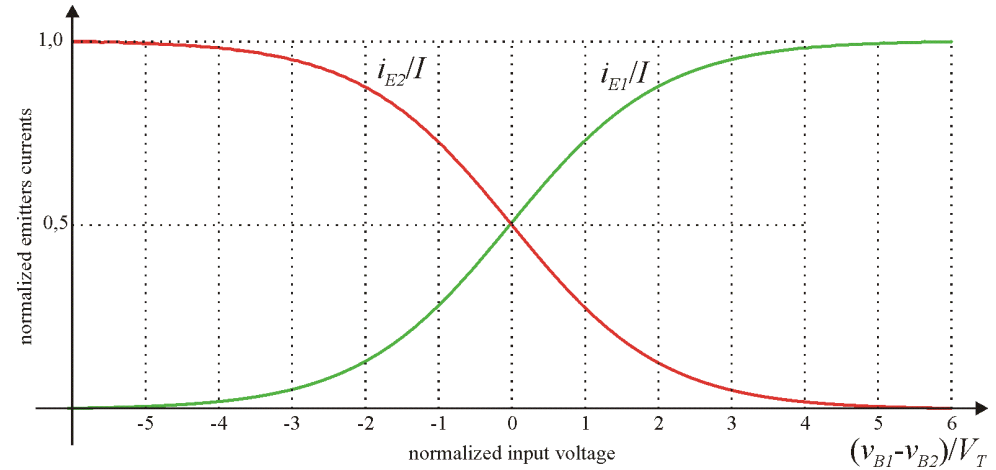

*Fig. 3. Normalized emitter currents of bipolar differential pair.*

Using substitution:  $\frac{v_{ID}}{V_T} = x = 2y$  a changeable part of the emitter current can be calculated as:

$$\begin{aligned} i_{E1} - \frac{I}{2} &= \frac{I}{1 + e^x} - \frac{I}{2} = \frac{I}{2} \left( \frac{e^x - 1}{e^x + 1} \right) = \frac{I}{2} \left( \frac{e^{2y} - 1}{e^{2y} + 1} \right) = \frac{I}{2} \left( \frac{e^{2y-y} - e^{-y}}{e^{2y-y} + e^{-y}} \right) \\ &= \frac{I}{2} \left( \frac{e^y - e^{-y}}{e^y + e^{-y}} \right) = \frac{I}{2} \tanh(y) = \frac{I}{2} \tanh\left(\frac{v_{ID}}{2V_T}\right) \end{aligned} \quad \text{and:}$$

$$i_{E2} - \frac{I}{2} = -\frac{I}{2} \tanh(y) = -\frac{I}{2} \tanh\left(\frac{v_{ID}}{2V_T}\right) \quad 9$$

# Bipolar differential pair, cont.

The difference of emitter currents is therefore equal to:

$$i_{E1} - i_{E2} = I \tanh(y) = I \tanh\left(\frac{v_{ID}}{2V_T}\right)$$

The difference of collector currents will be equal:

$$i_{C1} - i_{C2} = \alpha I \tanh(y) = \alpha I \tanh\left(\frac{v_{ID}}{2V_T}\right)$$

If we treat current  $I$  as one of the processed signals, then we obtain the multiplication of the term  $\tanh(x)$  and the current  $I$ . The term  $\tanh(x)$ , for a strong limitation of  $x \ll 1$  (i.e. for  $v_{ID} \ll 2V_T$ ) can be approximated by a linear function.

$$\tanh(x) \approx x - \frac{x^3}{3} + \frac{2x^5}{15} - \frac{17x^7}{315} + \dots$$

So, if  $v_{ID} \ll 2V_T$  then:

$$i_{C1} - i_{C2} \approx \alpha I \left(\frac{v_{ID}}{2V_T}\right)$$

**NOTE: there are no even terms in the expansion of the output current into a power series – it results in reduced value of harmonic distortion.**

# Bipolar differential pair, cont.

We expand output current into a power series and limit to the 4th term:

$$i_{C1} - i_{C2} = \alpha I \tanh(y) = \alpha I \tanh\left(\frac{v_{ID}}{2V_T}\right) = \alpha I \left( \frac{v_{ID}}{2V_T} - \frac{1}{3} \left( \frac{v_{ID}}{2V_T} \right)^3 + \dots \right) \approx \alpha I \left( \frac{v_{ID}}{2V_T} + \frac{v_{ID}^3}{24V_T^3} \right)$$

$$i_{C1} - i_{C2} = f(v_{ID}) = K_0 + K_1 v_{IN} + K_2 v_{IN}^2 + K_3 v_{IN}^3 + K_4 v_{IN}^4$$

$$K_0 = 0 \quad K_1 = \frac{\alpha I}{2V_T} \quad K_2 = 0 \quad K_3 = -\frac{\alpha I}{24V_T^3} \quad K_4 = 0$$

$$\tanh(x) \approx x - \frac{x^3}{3} + \frac{2x^5}{15} - \frac{17x^7}{315} + \dots$$

$$HD_2 \approx \frac{1}{2} \frac{K_2}{K_1} B = 0$$

$$HD_3 \approx \frac{1}{4} \frac{K_3}{K_1} B^2 = \frac{1}{4} \frac{2V_T}{24V_T^3} B^2 = \frac{1}{48V_T^2} B^2 \Rightarrow THD \approx HD_3 \Rightarrow B = \sqrt{48V_T^2 THD}$$

For example, for THD < 1%, the amplitude of the harmonic signal fed to the differential pair input must be:

$$B < \sqrt{48V_T^2 THD} = \sqrt{48 \cdot 25 [\text{mV}]^2 0,01} = 17,3 [\text{mV}]$$

# Bipolar differential pair, cont.

The gain of harmonic signals, which is transconductance for a differential pair, will be equal to:

$$GM_H = K_1 + \frac{3}{4} K_3 B^2 = \frac{\alpha I}{2V_T} - \frac{3}{4} \frac{\alpha I}{24V_T^3} B^2$$

Denoting as low signal transconductance:  
we get:

$$gm = \frac{\alpha I}{2V_T}$$

$$GM_H = gm \left( 1 - \frac{1}{16V_T^2} B^2 \right)$$

The above calculations are valid as long as the higher order factors are not dominant, in order to calculate this we can apply the inequality:

$$\tanh(x) \approx x - \frac{x^3}{3} + \frac{2x^5}{15} - \frac{17x^7}{315} + \dots \quad \left| \frac{2x^5}{15} \right| \ll \left| -\frac{x^3}{3} \right| \Rightarrow |x| \ll \sqrt{5/2}$$

Because:  $x = \frac{v_{ID}}{2V_T}$  so:  $|v_{ID}| \ll 2V_T \sqrt{5/2} = 80[\text{mV}]$

In practice, due to the quadratic relationship between terms of 5 and 3 order limitation  $v_{ID} < 2V_T$  is enough.

# Bipolar differential pair as a simple multiplier.

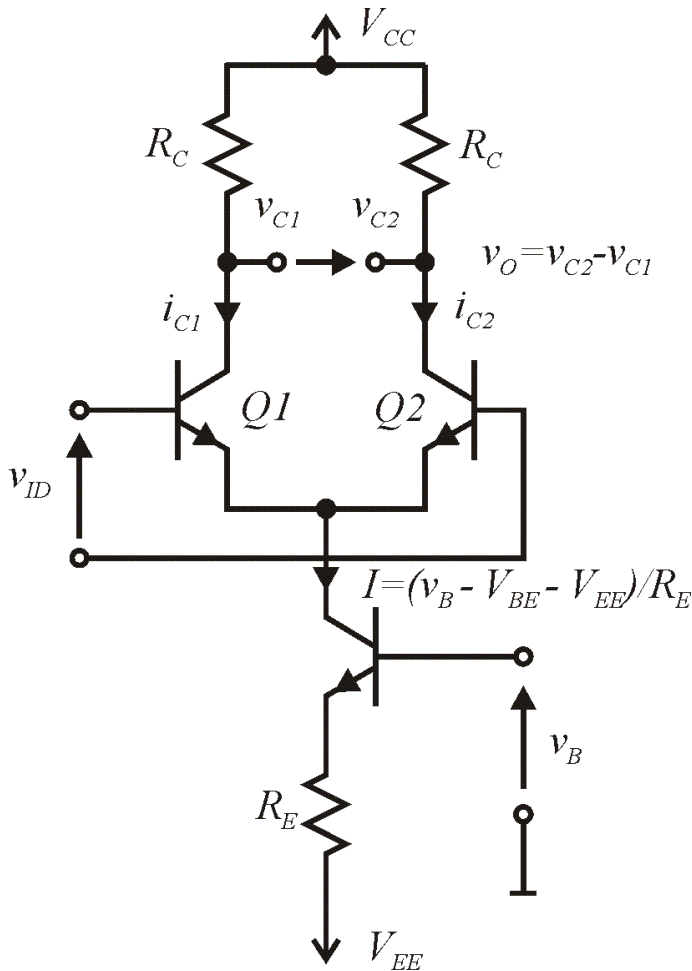


Fig. 4. Bipolar differential pair with current source implemented on Q3 transistor.

The difference of collector currents is equal to:

$$i_{C1} - i_{C2} = \alpha I \tanh\left(\frac{v_{ID}}{2V_T}\right) = \alpha \frac{v_B - V_{BE} - V_{EE}}{R_E} \tanh\left(\frac{v_{ID}}{2V_T}\right)$$

$$= \alpha \frac{v_B}{R_E} \tanh\left(\frac{v_{ID}}{2V_T}\right) + \alpha \frac{-V_{BE} - V_{EE}}{R_E} \tanh\left(\frac{v_{ID}}{2V_T}\right)$$

The output voltage is equal:

$$v_O = v_{C2} - v_{C1} = V_{CC} - i_{C2}R_C - (V_{CC} - i_{C1}R_C)$$

$$= i_{C1}R_C - i_{C2}R_C = (i_{C1} - i_{C2})R_C$$

And so:

$$v_O = \alpha \frac{v_B}{R_E} \tanh\left(\frac{v_{ID}}{2V_T}\right) R_C \quad \leftarrow \text{multiplication}$$

$$+ \alpha \frac{-V_{BE} - V_{EE}}{R_E} \tanh\left(\frac{v_{ID}}{2V_T}\right) R_C \quad \leftarrow \text{gain}_{13}$$

# Gilbert multiplier cell

For simplicity,  $\alpha = 1$  is assumed, so the collector currents are equal to the emitter currents.

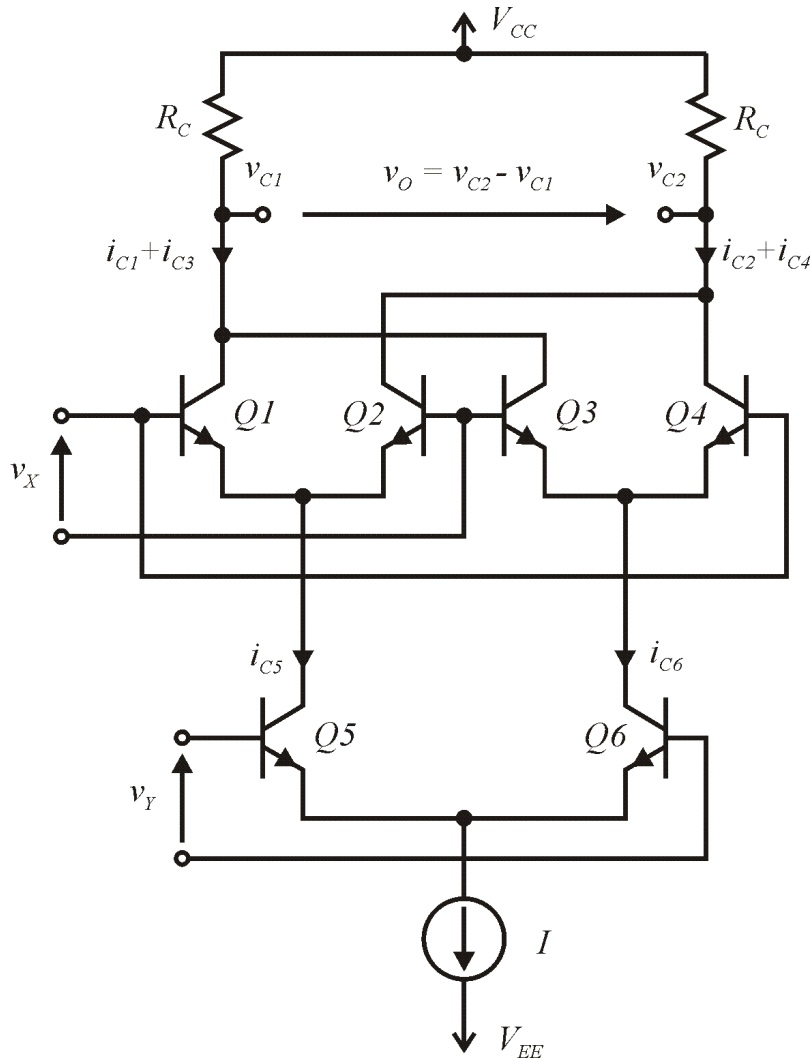


Fig. 5. Gilbert multiplier cell.

$$i_o = (i_{C1} + i_{C3}) - (i_{C2} + i_{C4}) = (i_{C1} - i_{C2}) - (i_{C4} - i_{C3})$$

$$= i_{C5} \tanh\left(\frac{v_X}{2V_T}\right) - i_{C6} \tanh\left(\frac{v_X}{2V_T}\right)$$

$$= (i_{C5} - i_{C6}) \tanh\left(\frac{v_X}{2V_T}\right)$$

$$= I \tanh\left(\frac{v_X}{2V_T}\right) \tanh\left(\frac{v_Y}{2V_T}\right)$$

$$= \begin{cases} \tanh(x) \approx x - \frac{x^3}{3} + \frac{2x^5}{15} - \frac{17x^7}{315} + \dots \\ v_X \ll 2V_T; v_Y \ll 2V_T \end{cases} = I \left(\frac{v_X}{2V_T}\right) \left(\frac{v_Y}{2V_T}\right)$$

$$\tanh(x) \approx x - \frac{x^3}{3} + \frac{2x^5}{15} - \frac{17x^7}{315} + \dots$$

$$v_o = v_{C2} - v_{C1}$$

$$= V_{CC} - (i_{C2} + i_{C4})R_C - (V_{CC} - (i_{C1} + i_{C3})R_C)$$


$$= (i_{C1} + i_{C3})R_C - (i_{C2} + i_{C4})R_C = i_o R_C$$

$$\approx I \left(\frac{v_X}{2V_T}\right) \left(\frac{v_Y}{2V_T}\right) R_C = K_V v_X v_Y$$

# Multiplier – increasing the linearity range for the Y input

For the circuits shown below, assuming that the  $v_Y$  signal passes to the emitters of the transistors without reducing the value, the collector currents are equal to:

$$i_{C5} = \frac{I}{2} + \frac{v_Y}{R_Y} \quad i_{C6} = \frac{I}{2} - \frac{v_Y}{R_Y} \quad i_{C5} - i_{C6} = 2 \frac{v_Y}{R_Y} \quad i_O = (i_{C5} - i_{C6}) \tanh\left(\frac{v_X}{2V_T}\right) = 2 \frac{v_Y}{R_Y} \tanh\left(\frac{v_X}{2V_T}\right) = \left|_{v_X \ll 2V_T} \frac{v_X}{V_T} \frac{v_Y}{R_Y}\right.$$

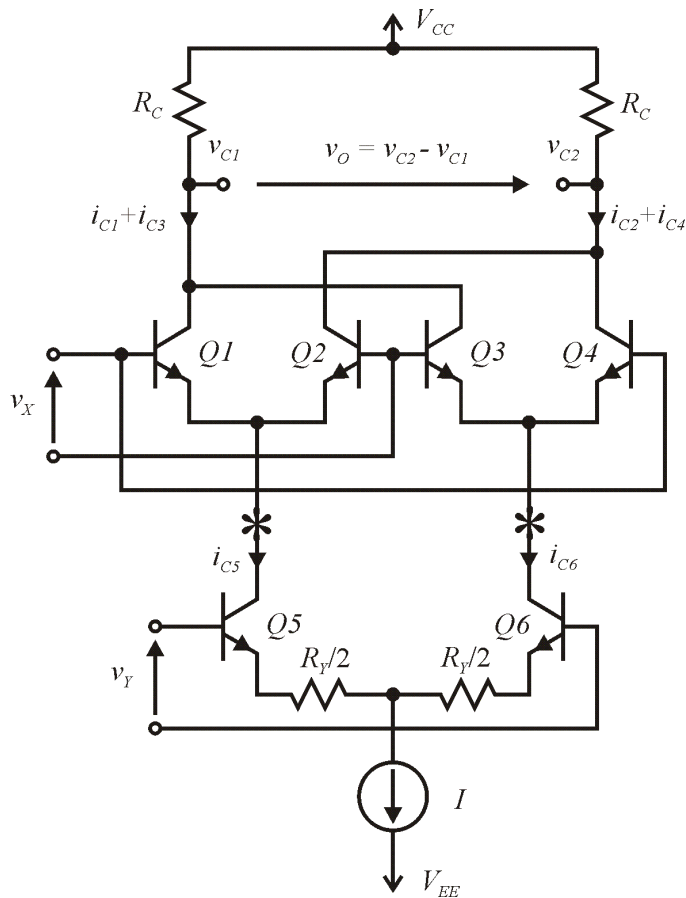

The condition of the 1: 1 signal transition to the Q5 and Q6 emitters (derived from the small signal  $T$  model of BJT):

$$\frac{R_Y}{2} \gg r_{e5,6} \Rightarrow \frac{R_Y}{2} \gg \frac{V_T}{I/2} \Rightarrow R_Y \gg 4 \frac{V_T}{I}$$

The condition of not draining the  $I/2$  current:

$$\frac{I}{2} > \left| \frac{v_Y}{R_Y} \right| \Rightarrow |v_Y| < \frac{1}{2} I R_Y$$

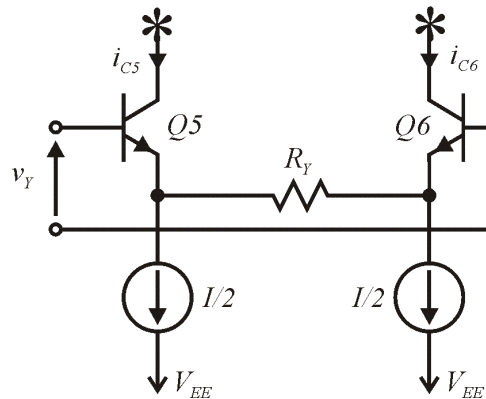


Fig. 6. Increasing the linearity range for the Y input of the Gilbert cell.

# Gilbert multiplier - increasing the linearity range for both inputs

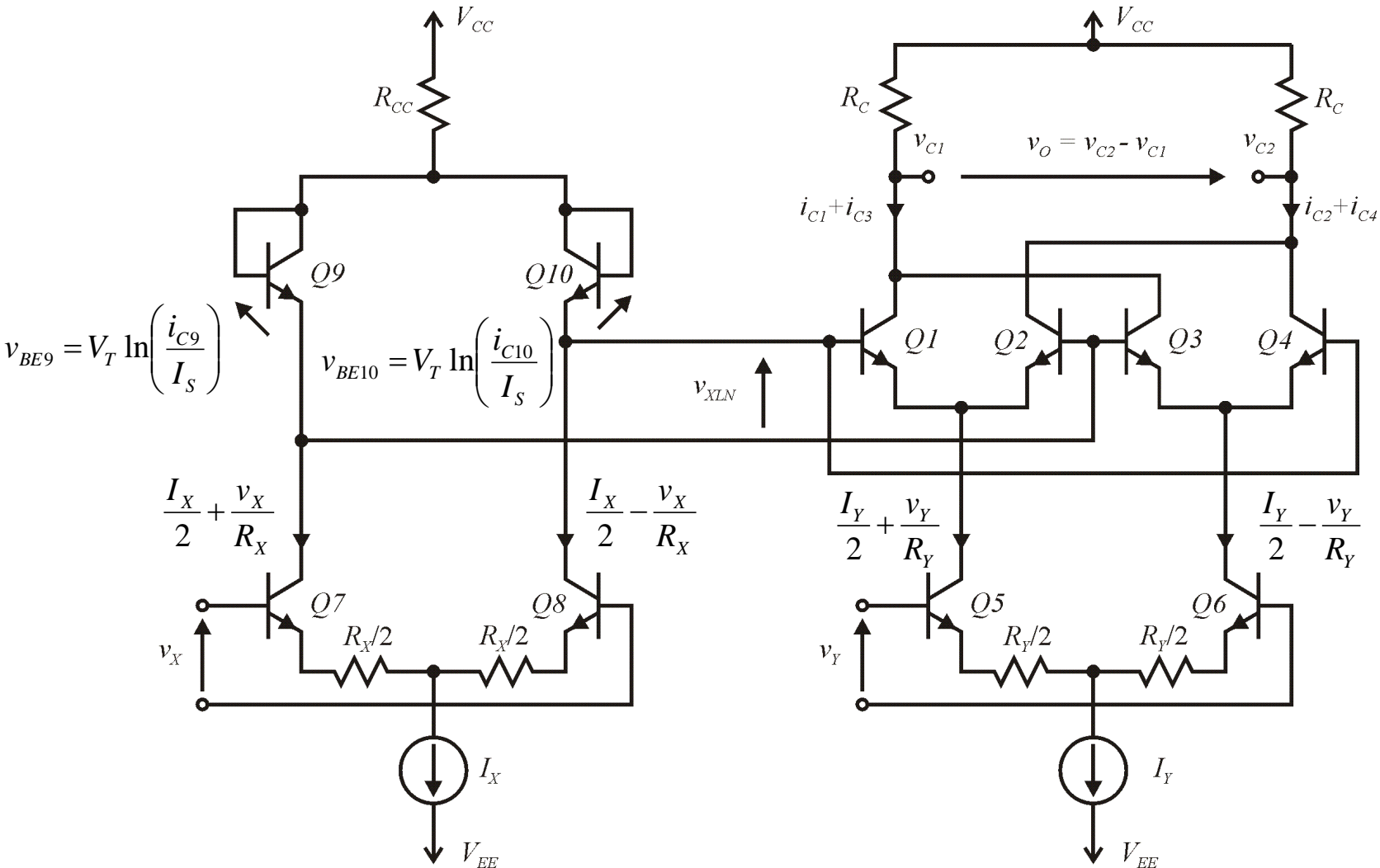


Fig. 7. Gilbert multiplier with both inputs linearisation.



For simplicity,  $\alpha=1$  was used, so the collector currents are equal to the emitter currents. It was assumed that the transistors are identical in pairs. The base-emitter voltage can be estimated as:

$$i_C = I_S e^{\frac{v_{BE}}{V_T}} \Rightarrow v_{BE} = V_T \ln \frac{i_C}{I_S}$$

For voltage designated as  $v_{XLN}$ , one can arrange Kirchhoff's voltage laws:

$$v_{XLN} = v_{BE1} - v_{BE2} = v_{BE9} - v_{BE10}$$

$$v_{XLN} = v_{BE4} - v_{BE3} = v_{BE9} - v_{BE10}$$

So:

$$V_T \ln \frac{i_{C1}}{I_{S1}} - V_T \ln \frac{i_{C2}}{I_{S2}} = V_T \ln \frac{i_{C9}}{I_{S9}} - V_T \ln \frac{i_{C10}}{I_{S10}} \Rightarrow \ln \frac{i_{C1}}{i_{C2}} = \ln \frac{i_{C9}}{i_{C10}} \Rightarrow \frac{i_{C1}}{i_{C2}} = \frac{i_{C9}}{i_{C10}}$$

Substituting to the above equation and finding the difference in currents we get:

$$i_{C9} = I_X/2 + v_X/R_X$$

$$i_{C10} = I_X/2 - v_X/R_X$$

$$i_{C1} - i_{C2} = i_{C5} \left( \frac{2}{I_X} \frac{v_X}{R_X} \right)$$

Similarly, for Q3 and Q4 pair their current difference can be defined as:

$$i_{C4} - i_{C3} = i_{C6} \left( \frac{2}{I_X} \frac{v_X}{R_X} \right)$$

Hence, the output current being the difference of the currents of the respective pairs is equal to:

$$\begin{aligned}
 i_o &= (i_{C1} + i_{C3}) - (i_{C2} + i_{C4}) = (i_{C1} - i_{C2}) - (i_{C4} - i_{C3}) = i_{C5} \left( \frac{2}{I_X} \frac{v_X}{R_X} \right) - i_{C6} \left( \frac{2}{I_X} \frac{v_X}{R_X} \right) \\
 &= (i_{C5} - i_{C6}) \left( \frac{2}{I_X} \frac{v_X}{R_X} \right) = \left( 2 \frac{v_Y}{R_Y} \right) \left( \frac{2}{I_X} \frac{v_X}{R_X} \right) = v_X v_Y \frac{4}{I_X R_X R_Y}
 \end{aligned}$$

The above relationship is limited for input voltages that zeroes one of the lower differential pair currents, i.e. for input voltages in the range:

$$\frac{I_X}{2} > \left| \frac{v_X}{R_X} \right| \Rightarrow |v_X| < \frac{1}{2} I_X R_X \quad \frac{I_Y}{2} > \left| \frac{v_Y}{R_Y} \right| \Rightarrow |v_Y| < \frac{1}{2} I_Y R_Y$$

The output voltage, similarly to previous circuits, can be determined as:

$$\begin{aligned}
 v_o &= v_{C2} - v_{C1} = V_{CC} - (i_{C2} + i_{C4})R_C - (V_{CC} - (i_{C1} + i_{C3})R_C) \\
 &= (i_{C1} + i_{C3})R_C - (i_{C2} + i_{C4})R_C = i_o R_C = v_X v_Y \frac{4}{I_X R_X R_Y} R_C = K_V v_X v_Y
 \end{aligned}$$

$$K_V = \frac{4R_C}{I_X R_X R_Y}$$

# Differential current converter circuit

For the circuit as shown in the scheme, current Kirchhoff's law in the input nodes of operational amplifier  $A$  can be written as:


$$\frac{V_{CC} - v_-}{R_{C1}} + \frac{v_o - v_-}{R_{F1}} = i_1 \quad \frac{V_{CC} - v_+}{R_{C2}} = \frac{v_+}{R_{F2}} + i_2$$

If we assume the equality of resistors

$$R_{C1} = R_{C2} = R_C \quad \text{and} \quad R_{F1} = R_{F2} = R_F$$

and ideal amplifier  $A$ , then the output voltage is equal to:

$$v_o = (i_1 - i_2)R_F$$

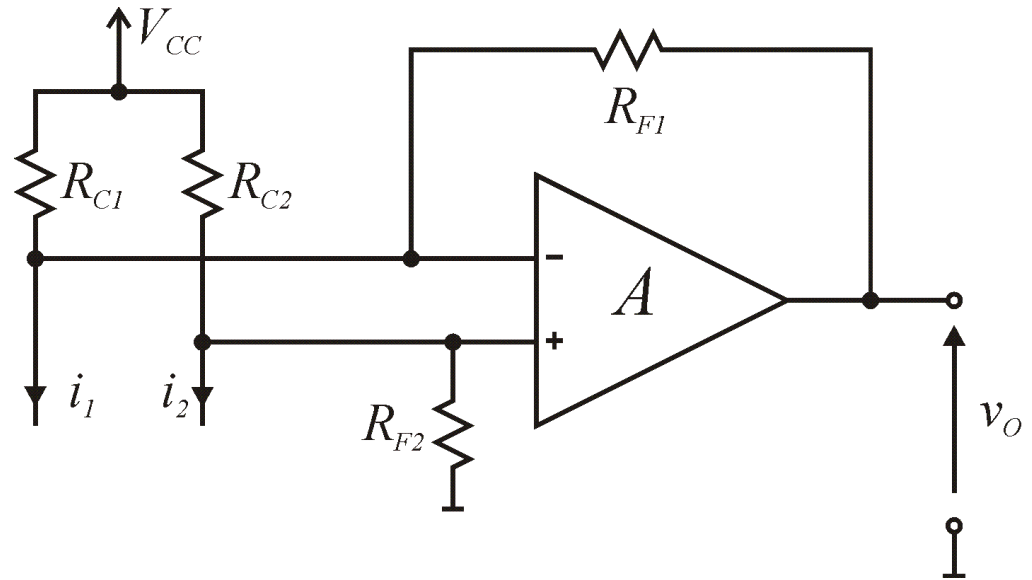

*Fig. 8. Differential current to single output voltage converter.*

$$v_{OUT} = i_O R_F = v_X v_Y \frac{4}{I_X R_X R_Y} R_F$$

$$K_V = \frac{4R_F}{I_X R_X R_Y}$$

$$v_O \neq i_O R_C$$

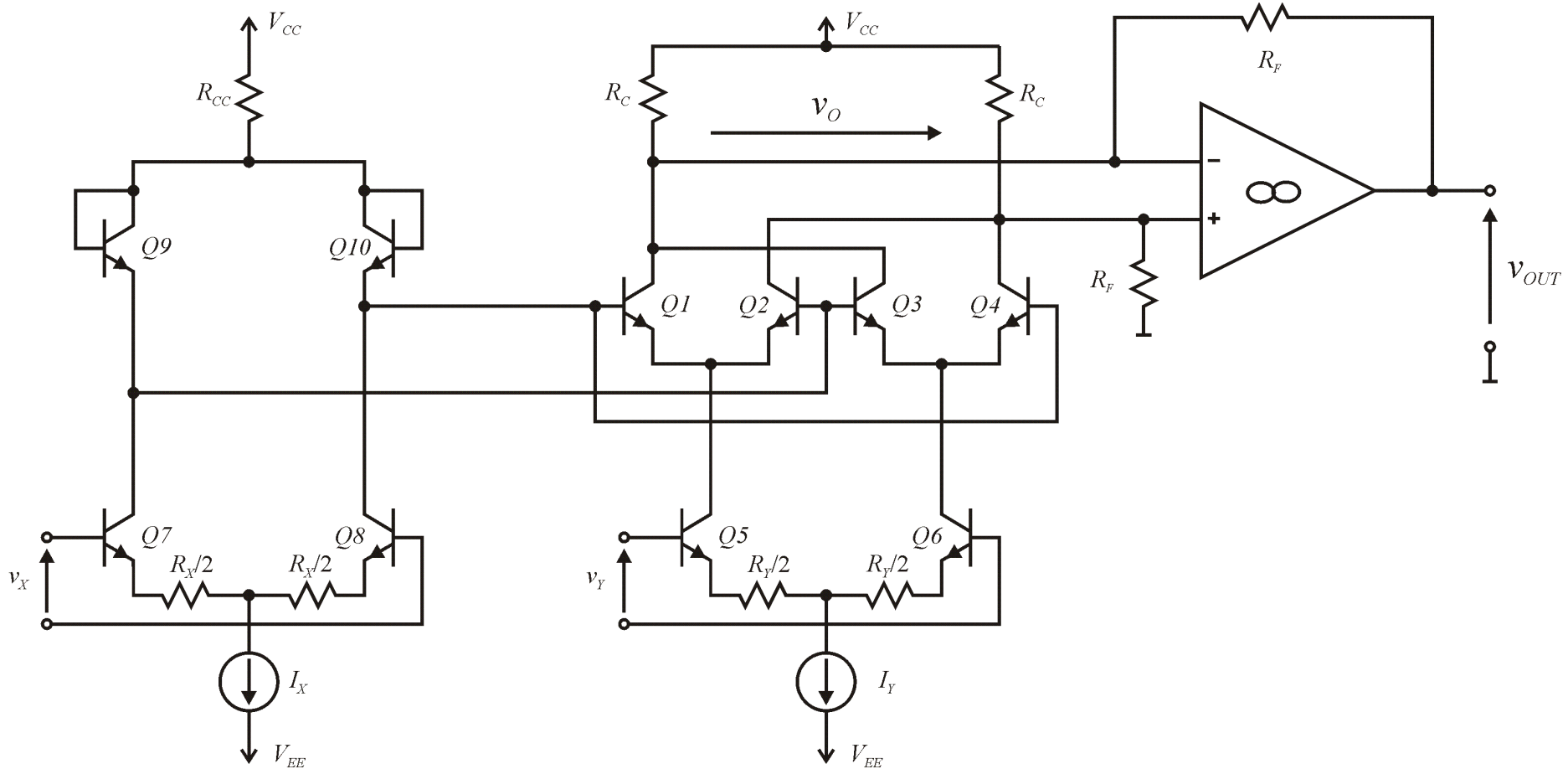


Fig. 9. Linearized four-quadrant Gilbert multiplier with voltage output.


# Implementation of selected non-linear functions

- Division
- Square up
- Square root
- Logarithm
- Exponential circuit

# Ideal Operational Amplifier

## virtual short circuit rule

For an ideal OA, differential gain  $A_D$  tends to infinity. Let's assume that OA works in negative feedback loop as e.g. in the picture below.

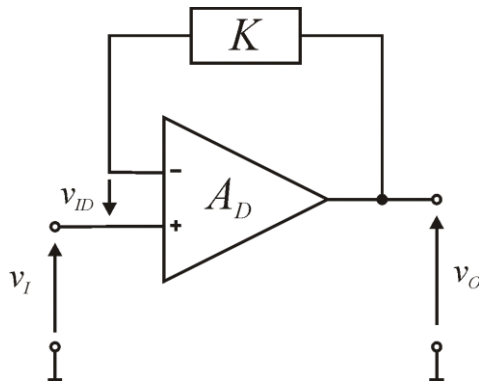

*Fig. 11. Operational amplifier with negative feedback loop K.*


Circuit equations for the above case:

$$v_O = A_D v_{ID} = A_D (v_I - v_O K) \Rightarrow v_O (1 + A_D K) = A_D v_I \Rightarrow v_O = v_I \frac{A_D}{1 + A_D K} \Big|_{A_D \rightarrow \infty} = v_I / K$$

And what is the value of differential input voltage?

$$v_{ID} = \frac{v_O}{A_D} = \frac{v_I \frac{A_D}{1 + A_D K}}{A_D} = v_I \frac{1}{1 + A_D K} \Big|_{A_D K \rightarrow \infty} = 0$$

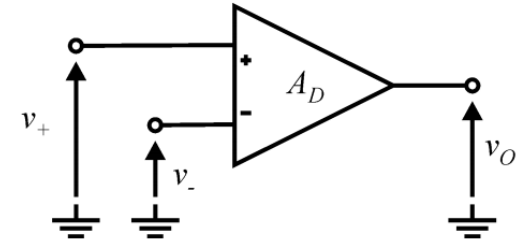**In an ideal OA with negative feedback loop the voltage difference between the inputs tends to zero, which in practice means a "virtual" short circuit between the amplifier's inputs**



$$v_O = A_D (v_+ - v_-) \quad v_{ID} = v_+ - v_-$$

*Fig. 10. Operational Amplifier (OA) symbol.*

# Division

Assuming negative feedback loop input voltage  $v_Y$  is limited to positive values. For ideal OA:

$$i_{R1} = \frac{v_X}{R_1} = \frac{-K_V v_Y v_O}{R_2} \Rightarrow v_O = -\frac{R_2}{K_V v_Y} \frac{v_X}{R_1} = -\frac{R_2}{K_V R_1} \frac{v_X}{v_Y}$$


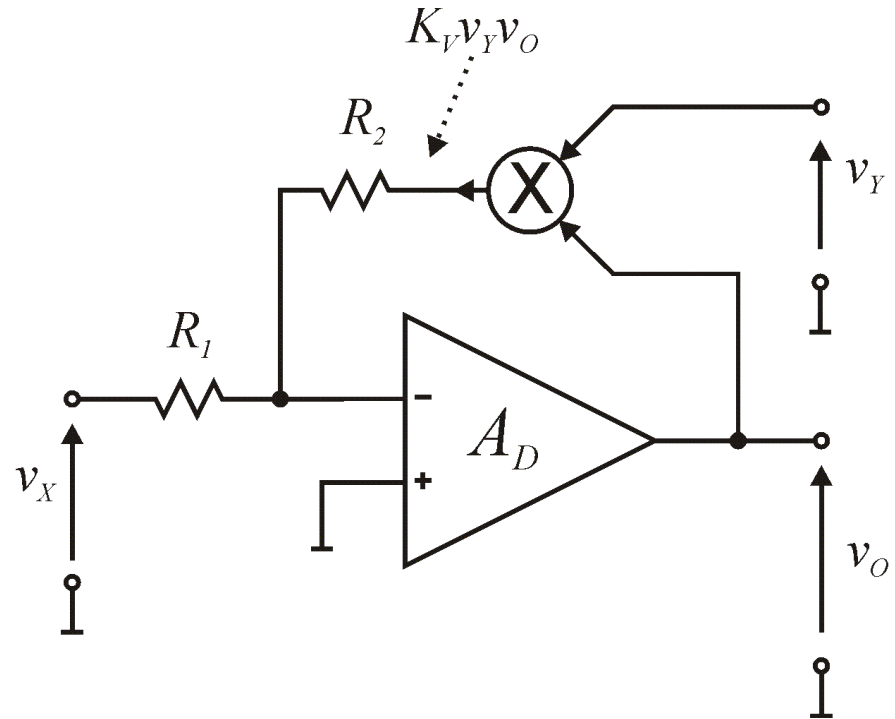


Fig. 12. Division circuit.

# Square up

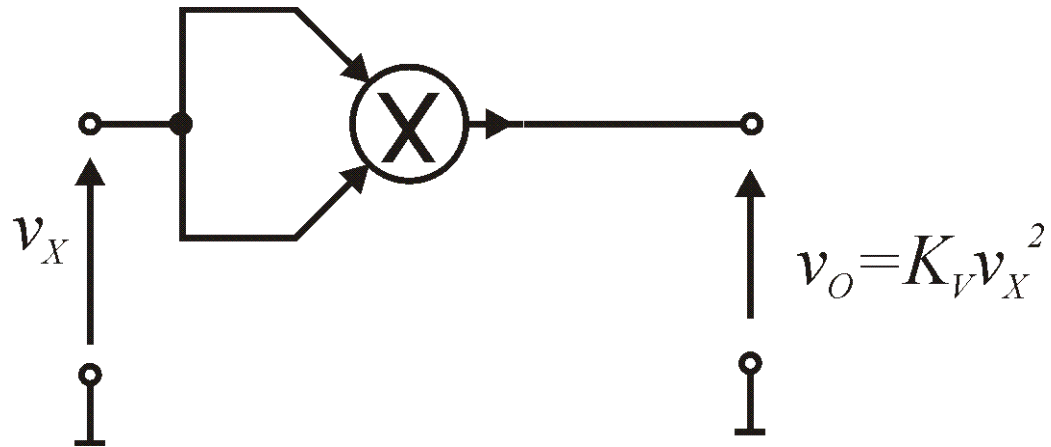

*Fig. 13. Square up circuit with the use of multiplier.*



# Square root

Assuming the negative feedback loop the output voltage  $v_o$  is limited to positive values, so the input voltage must be negative! Current equation assuming ideal OA:

$$i_{R1} = -\frac{v_X}{R_1} = \frac{K_V v_o^2}{R_2} \Rightarrow v_o = \sqrt{-v_X \frac{R_2}{K_V R_1}}$$

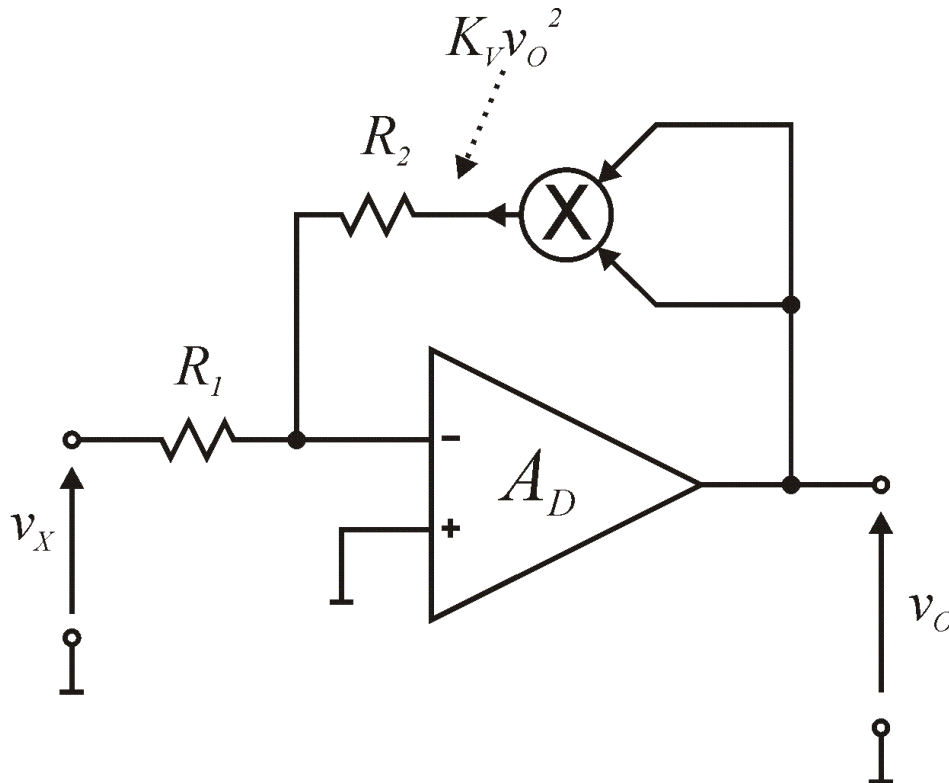


Fig. 15. Square root circuit.

# Logarithm

Assuming negative feedback loop and positive collector current input voltage  $v_X$  is limited to positive values. For ideal OA:

$$i_{R1} = \frac{v_X}{R_1} = i_C = I_S e^{\frac{v_{BE}}{V_T}} = I_S e^{\frac{-v_O}{V_T}} \Rightarrow \ln\left(\frac{v_X}{I_S R_1}\right) = \frac{-v_O}{V_T} \Rightarrow v_O = -V_T \ln\left(\frac{v_X}{I_S R_1}\right)$$


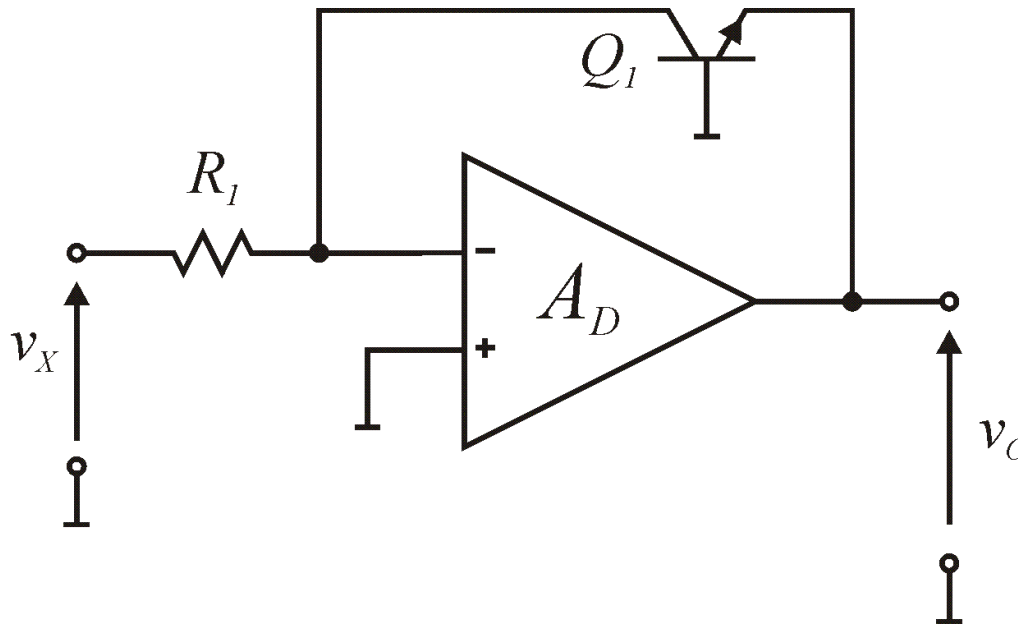


Fig. 16. Logarithm circuit.
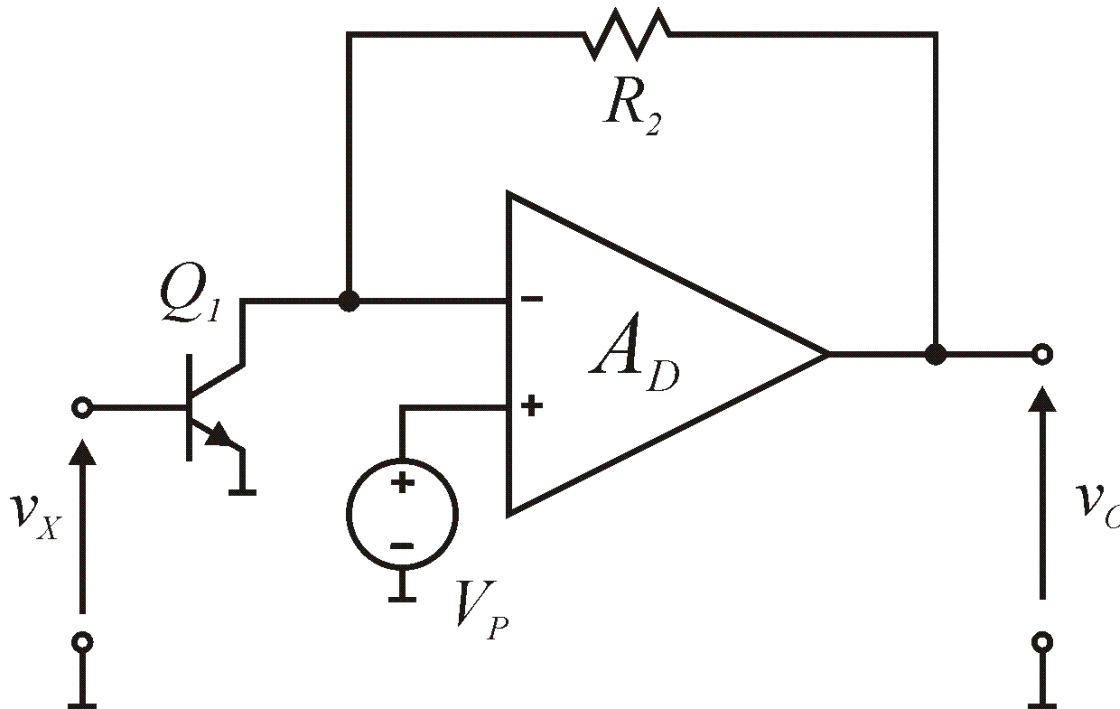
# Exponential circuit

Assuming negative feedback loop and positive collector current input voltage  $v_X$  is limited to positive values. For ideal OA:

$$i_{R_2} = \frac{v_O - V_P}{R_2} = i_C = I_S e^{\frac{v_{BE}}{V_T}} = I_S e^{\frac{v_X}{V_T}} \Rightarrow v_O = R_2 I_S e^{\frac{v_X}{V_T}} + V_P$$



Due to the necessity to force the NPN transistor to work in the active normal range it is necessary to apply polarizing voltage  $V_P$ ,  $v_{CE} = V_P$ .

Fig. 17. Exponential circuit.