

AKADEMIA ETI 2012



PLAN WYKŁADU

- SYSTEMY LICZBOWE;
- ALGEBRA BOOLA;
- BRAMKI LOGICZNE;
- TABLICE KARNAUGH;
- UKŁADY LOGICZNE;

SYSTEM DZIESIĘTNY

- WYKORZYSTYWANE SYMBOLE:
0, 1, 2, 3, 4, 5, 6, 7, 8, 9;
- $4532 = 2 \cdot 10^0 + 3 \cdot 10^1 + 5 \cdot 10^2 + 4 \cdot 10^3$
- $498 = 8 \cdot 10^0 + 9 \cdot 10^1 + 4 \cdot 10^2$
- $12 = 2 \cdot 10^0 + 1 \cdot 10^1$

SYSTEM BINARNY

- WYKORZYSTYWANE SYMBOLE:
0, 1;
- $10010 = 0*2^0 + 1*2^1 + 0*2^2 + 0*2^3 + 1*2^4$
- $1011 = 1*2^0 + 1*2^1 + 0*2^2 + 1*2^3$
- $101 = 1*2^0 + 0*2^1 + 1*2^2$

KONWERSJA LICZB

| | | | |
|-----|---|-----|---|
| 123 | 1 | 129 | 1 |
| 61 | 1 | 64 | 0 |
| 30 | 0 | 32 | 0 |
| 15 | 1 | 16 | 0 |
| 7 | 1 | 8 | 0 |
| 3 | 1 | 4 | 0 |
| 1 | 1 | 2 | 0 |
| 0 | | 1 | 1 |
| | | 0 | |

KOD GRAYA

| DECIMAL | BINARY | GRAY |
|---------|--------|------|
| 0 | 000 | 000 |
| 1 | 001 | 001 |
| 2 | 010 | 011 |
| 3 | 011 | 010 |
| 4 | 100 | 110 |
| 5 | 101 | 111 |
| 6 | 110 | 101 |
| 7 | 111 | 100 |

ALGEBRA BOOLA [1]

$$x + 0 = x$$

$$x + 1 = 1$$

$$x + x = x$$

$$x + \overline{x} = 1$$

$$x + x * y = x * (1 + y) = x * 1 = x$$

$$x + \overline{x} * y = (x + \overline{x})(x + y) = x + y$$

$$\overline{(x + y)} = \overline{x} * \overline{y}$$

$$\overline{(x + y + z)} = \overline{x} * \overline{y} * \overline{z}$$

ALGEBRA BOOLA [1]

$$x * 0 = 0$$

$$x * 1 = x$$

$$x * x = x$$

$$x * \bar{x} = 0$$



$$x * (x + y) = x + x * y = x$$

$$x * (\bar{x} + y) = x * y$$

$$\overline{(x * y)} = \bar{x} + \bar{y}$$

$$\overline{(x * y * z)} = \bar{x} + \bar{y} + \bar{z}$$



BUFOR, INWERTER [2]

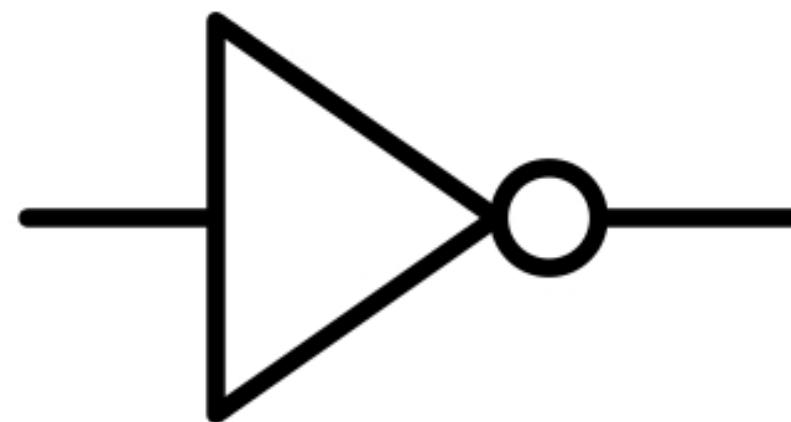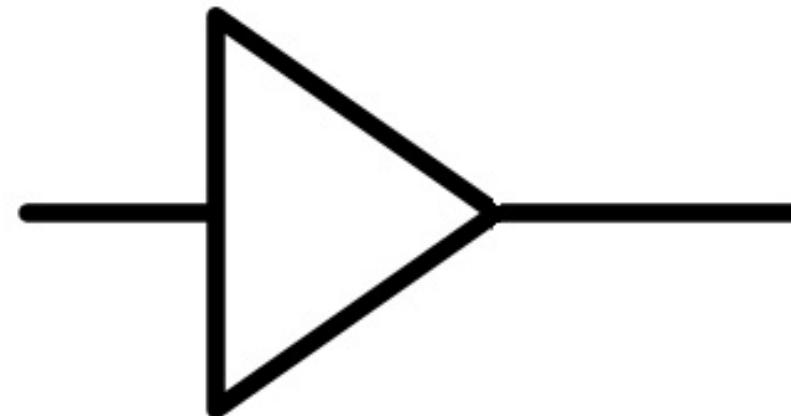

| A | Y |
|---|---|
| 0 | 0 |
| 1 | 1 |

| A | Y |
|---|---|
| 0 | 1 |
| 1 | 0 |



AND, NAND [2]

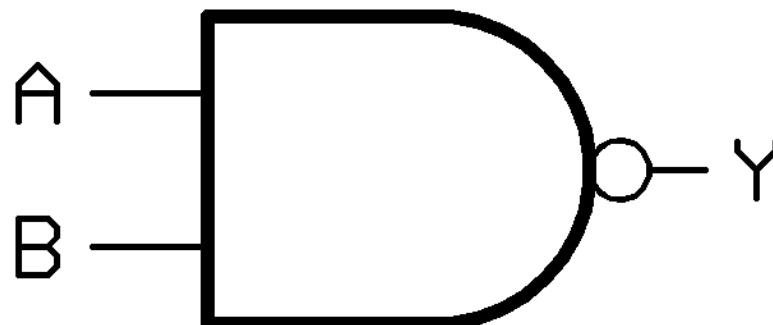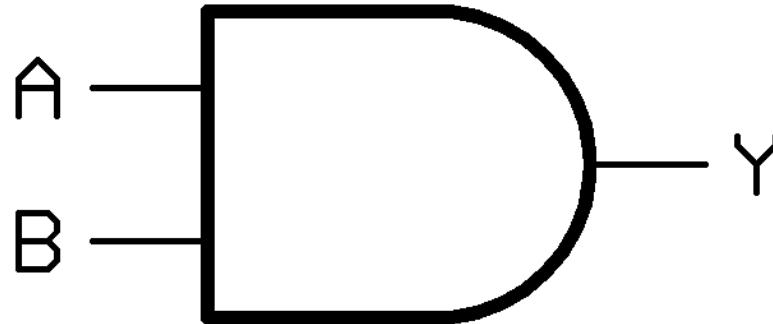

| A | B | Y |
|---|---|---|
| 0 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

| A | B | Y |
|---|---|---|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |



OR, NOR [2]

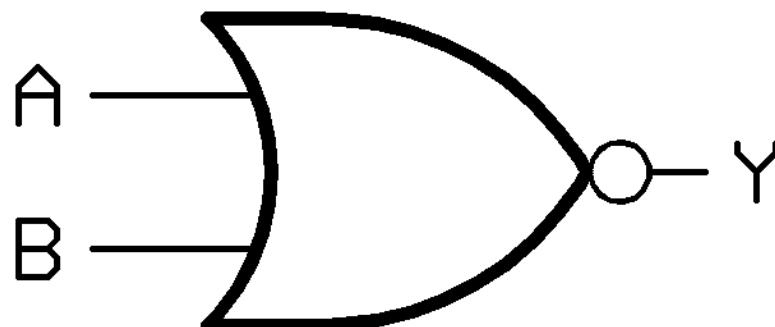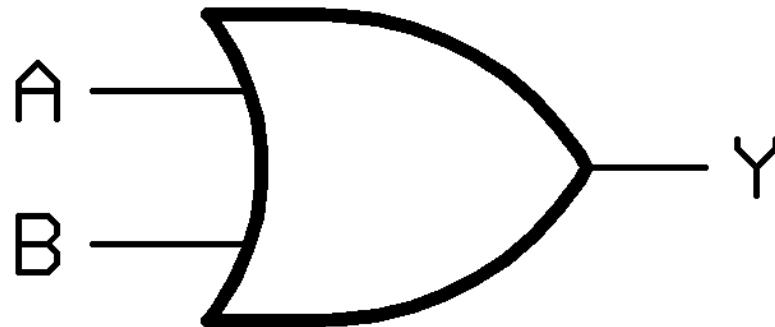

| A | B | Y |
|---|---|---|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 1 |

| A | B | Y |
|---|---|---|
| 0 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

XOR, XNOR [2]

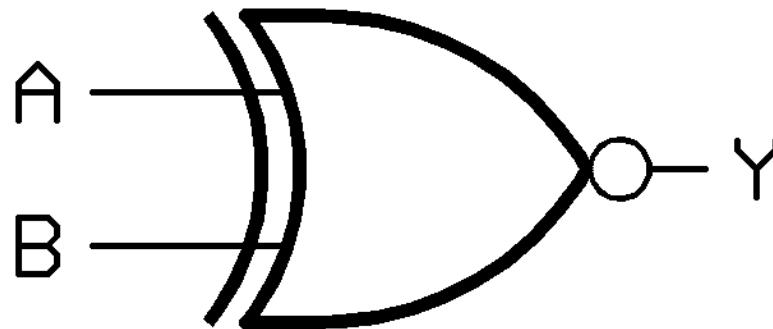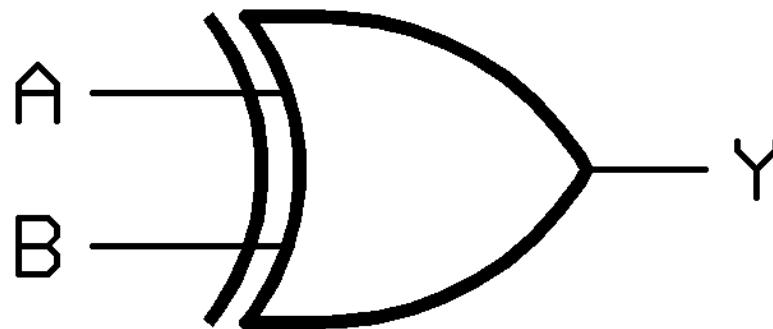

| A | B | Y |
|---|---|---|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |


| A | B | Y |
|---|---|---|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

TABLICE KARNAUGH


- **Przykład:**

„Zaprojektuj kombinacyjny układ sumatora dwóch 2-bitowych liczb binarnych.”


LOGIKA DYSKRETNNA [3]

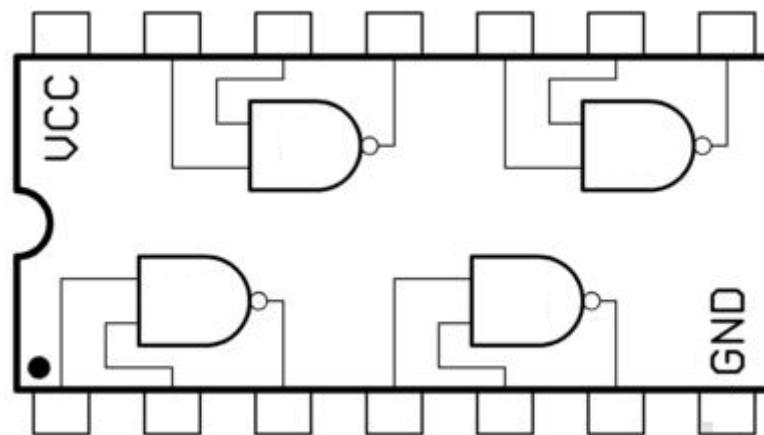

LOGIKA DYSKRETNNA [4]

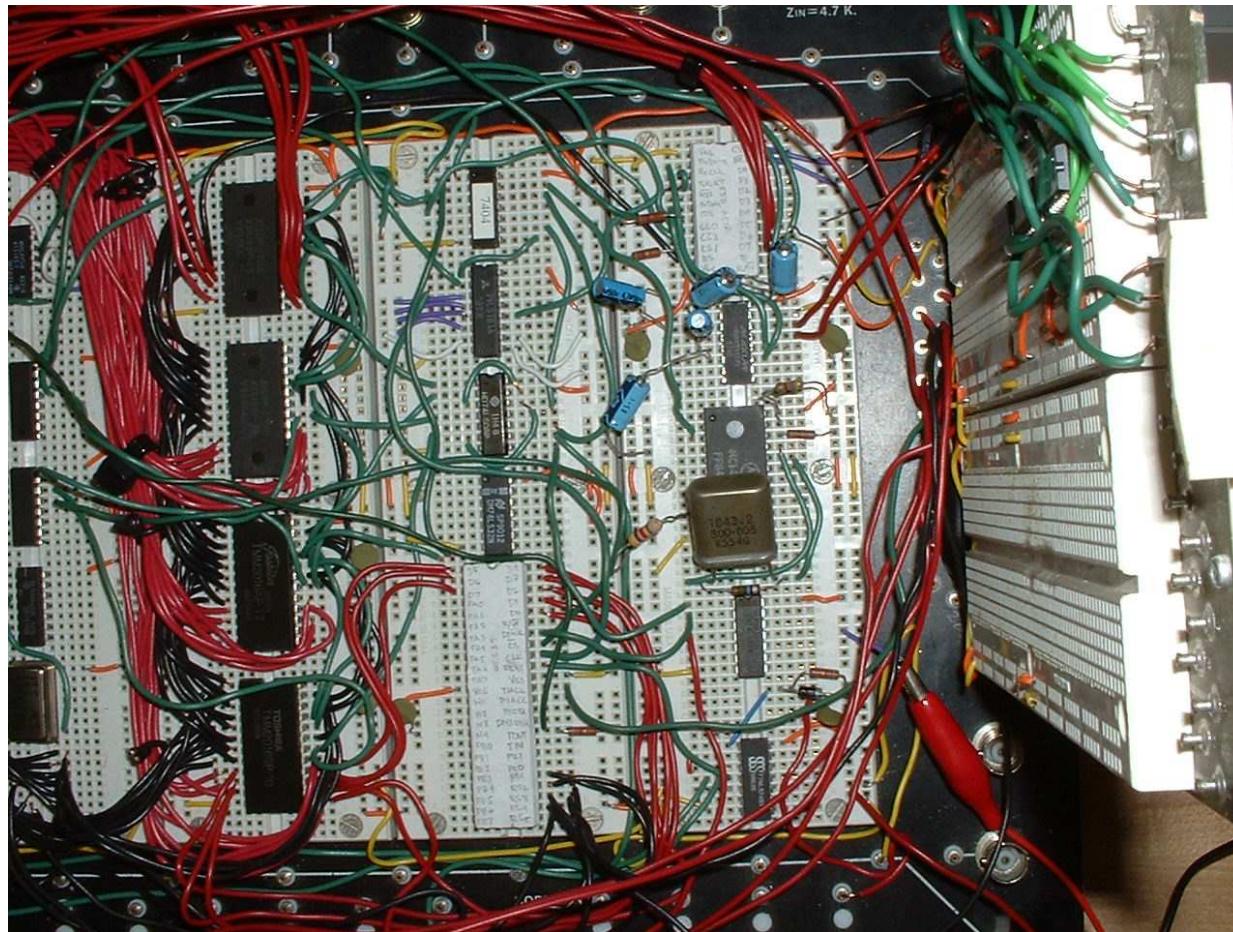

FPGA [5]

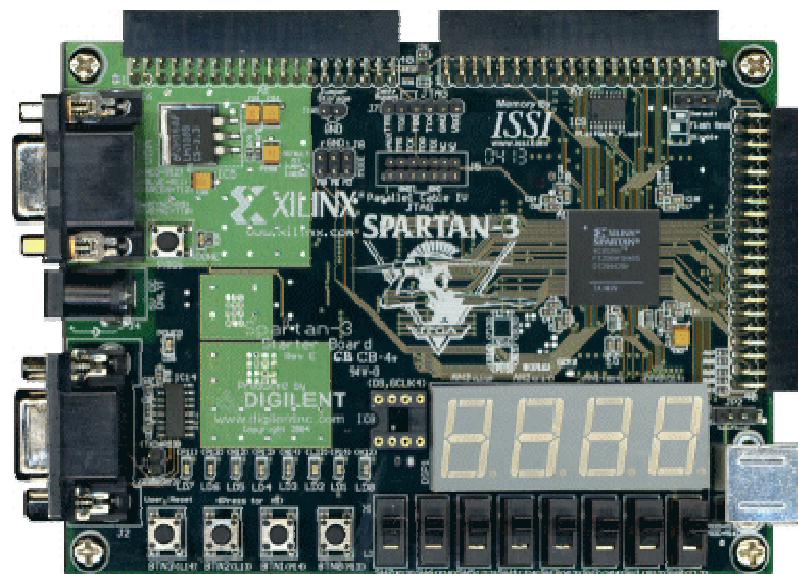

DZIĘKUJĘ ZA UWAGĘ

- [1] <http://galaxy.uci.agh.edu.pl/~jamro/tul/bool.pdf>
- [2] <http://commons.wikimedia.org/>
- [3] <http://dlnmh9ip6v2uc.cloudfront.net/tutorialimages/LogicBlocksExp/7400n-detailed.png>
- [4] <http://en.wikipedia.org/>
- [5] <http://www.digilentinc.com/>